



Course Code: CS203

Course Name: SWITCHING THEORY AND LOGIC DESIGN

Max. Marks: 100

Duration: 3 Hours

PART A

Answer all questions, each carries 3 marks.

		Marks
1	Any three advantages of digital systems over analogue systems- 1 mark each	(3)
2	Each conversion- i)1266(1.5 marks) ii)01100111 (1.5 marks).	(3)
3	K-map contents- 1.5 mark each	(3)
4	Complement of $A+BC'(D+EF)'$ - 3 marks	(3)

PART B

Answer any two full questions, each carries 9 marks.

5	a)	(i) 1's complement of the binary number 1101.01- 0010.10 -2 marks. (ii) Compute 8's complement of the octal number 672.23-105.55 - 2 marks. (iii) Ans: 10EF Addition -3 marks.	(7)
	b)	Decimal number 6.25 in binary- 2 marks $6.25=110.01= 1.1001 \times 2^2$ Sign bit=1 Exponent - 000010 Mantissa-100100000	(2)
6		Tabulation-5 marks Prime Implicants- 1 mark Essential Prime Implicant- $x'z + xz'$ 2 marks Simplified Expression- 1 mark. Ans $x'z + xz'$	(9)
7	a)	i) canonical PoS- $\pi(0,4)$ -2.5 marks ii) standard PoS- $(x+z)(x+y)$ 2.5 marks	(5)
	b)	Subtraction using 10's complement addition- 4 marks Ans -834	(4)

PART C

Answer all questions, each carries 3 marks.		
8		master-slave J-K flip-flop realized using NOR and AND gates- 3 marks (3)
9		truth table of a 4x1 de-multiplexer -1.5 marks logic diagram- 1.5 marks. (3)
10		full-subtractor design - 2 marks implementation using a decoder and 1 OR gate - 1 mark (3)
11		half-adder expression- 1 mark Diagram using NAND gates- 2 marks (3)
PART D		
Answer any two full questions, each carries 9 marks.		
12	a)	Boolean functions using a 2X1 multiplexer and additional gates - 3 marks Any valid design can be given marks. (For eg using 2 2x 1 MUX with enable input , implementing 4 x 1 MUX with 2 x 1 MUX etc) (3)
	b)	Truth table- 1 mark Code converter simplification using K-map- 3 marks Le inputs be ABC outputs be C1C2 C3 $C1 = AC' + AB' + A'BC$ $C2 = B'C + B C'$ $C3 = B'C' + B C'$ Diagram- 2 marks (6)
13	a)	Consider the outputs of 2-bit subtractor Difference and Borrow . If they are equal comparator output for =1 . If difference < borrow Comparator output for <= 1 else comparator output for > = 1. Write the truth table - 1 mark. K-map design 2 marks. (3)
	b)	State table - 1 mark Simplification using K-map- 3 marks Diagram- 2 marks Inputs are A, B,x. Using K - Map $TA = A'x + Bx + AB'x'$ $TB = (A \text{ XOR } B)x + A'B'x'$ (6)
14		state table - 6 marks state diagram - 3 marks (9)
PART E		
Answer any four full questions, each carries 10 marks.		
15		Diagram- 5 marks Working of serial adder- 5 marks. (10)
16		State table - 1 marks Simplification using K-map- 6 marks $J2 = Q0'$, $K2 = Q1'$; $J1 = Q2'$, $K1 = Q2Q0$; $J0 = Q2$, $K0 = Q1Q2'$ Diagram- 3 marks (10)
17		mod-16 ripple up-counter using J-K flip-flops.- 4 marks mod-12 ripple counter- 6 marks. In mod 12 Q3Q2 output should be connected to NAND gate. Output of NAND gate connected to Clear input. (10)
18	a)	Any 3 differences- 1 mark each (3)
	b)	read-only memory and read-write memory- 2 marks each (4)
	c)	Fig represents mod 2 ripple counter. Its timing diagram- Q1-1.5 marks Q2-1.5 marks (3)
19	a)	PLA- 4 marks (4)
	b)	Simplification using K-map - 2 marks each Diagram- 2 marks (6)
20		Algorithms / Flowchart for floating point addition - 5 marks floating point subtraction - 5 marks (10)

