

Register No.: ..... Name: .....

**SAINTGITS COLLEGE OF ENGINEERING  
KOTTAYAM, KERALA**

(AN AUTONOMOUS COLLEGE AFFILIATED TO  
APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY, THIRUVANANTHAPURAM)

**FIRST SEMESTER B.TECH DEGREE EXAMINATION(R), FEBRUARY 2022**

**Course Code: 20EST130**

**Course Name: BASICS OF ELECTRICAL AND ELECTRONICS ENGINEERING**

**Max. Marks: 100**

**Duration: 3 Hours**

**PART I BASIC ELECTRICAL ENGINEERING**

*Part I to be answered in pages 1 to 15*

**PART A**

*(Answer all questions. Each question carries 4 marks)*

1. Four resistors, of ohmic values  $5\Omega$ ,  $10\Omega$ ,  $15\Omega$ , and  $20\Omega$  are connected in series and a 100 V source is applied across the combination. How is this voltage divided among the various resistors?
2. Compare electric and magnetic circuits (give any 4 points).
3. An alternating current is given by  $i = 141.4 \sin 314t$ . Find (i) the maximum value (ii) frequency (iii) the time period (iv) the instantaneous value when  $t$  is 3 ms.
4. The instantaneous voltage and current for an AC circuit are  $v = 155.6 \sin 377t$  V and  $i = 7.07 \sin (377t - 36.87^\circ)$  A. Represent these a) as complex exponentials and b) in phasor diagram.
5. Define active, reactive and apparent power. Draw the power triangle.

**PART B**

*(Answer one full question from each module, each question carries 10 marks)*


**MODULE I**

6. a) Three  $700\Omega$  resistors, all in parallel are to be connected to 210 V dc source. It is desired to limit the voltage across these resistors to 110 V by connecting a resistor in series with the parallel combination. Determine (a) the value of resistor, and (b) the total power drawn by the 210 V source. (5)
- b) Three resistances of  $20\Omega$  each are connected in star. Find the equivalent delta resistance. If the source of e.m.f. of 120 V is connected across any two terminals of the equivalent delta connected resistances, find the current supplied by the source. (5)

**OR**

7. a) State and explain Kirchoff's laws (4)
- b) Using Node voltage analysis, find the branch currents of the following figure. (6)

## 219A2

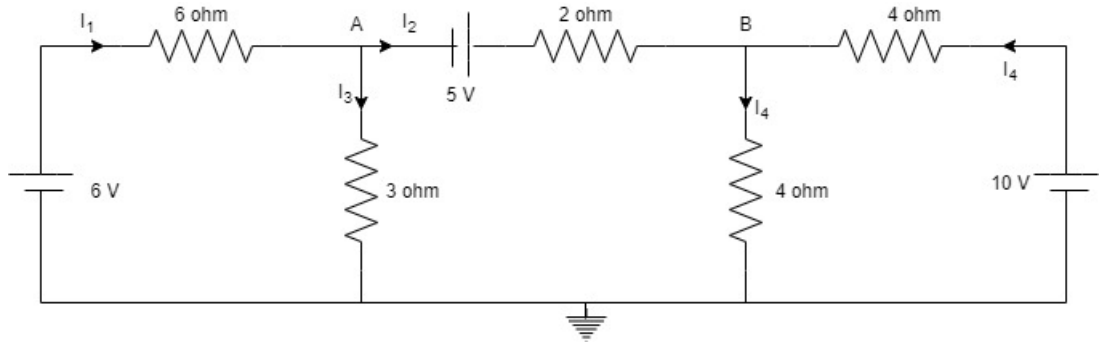


### MODULE II

8. a) Define self-inductance, mutual inductance and coefficient of coupling. (5)
- b) A resistance  $12 \Omega$ , an inductance of  $0.15 \text{ H}$  and a capacitance of  $100 \mu\text{F}$  are connected in series across a  $100 \text{ V}$ ,  $50 \text{ Hz}$  supply. Calculate :  
 (i) The current.  
 (ii) The phase difference between current and the supply voltage.  
 (iii) Power consumed. (5)  
 Draw the vector diagram of supply voltage and the line current.

### OR

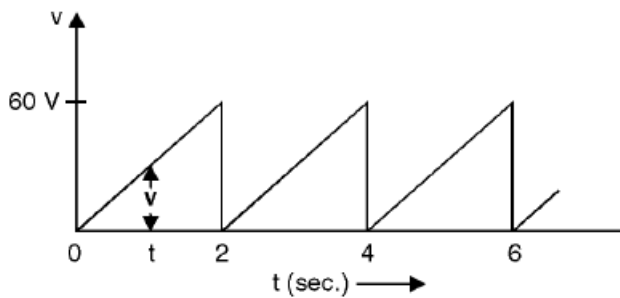9. a) Explain the following terms relating alternating current :  
 (i) R.M.S. value  
 (ii) Average value  
 (iii) Form factor. What is the form factor of a square wave (5)
- b) Determine the average and effective values of the saw-tooth waveform shown in figure.



### MODULE III

10. a) A series RLC circuit is excited by a  $100 \text{ V}$ ,  $79.6 \text{ Hz}$  source and has the following data:  $R = 100 \Omega$ ,  $L = 1 \text{ H}$ ,  $C = 5 \mu\text{F}$ . Calculate (a) the input current, and (b) the voltages across the elements. (8)
- b) Define power factor. What will be the power factor for a purely inductive circuit. (2)
- OR**
11. a) Derive the numerical relationship between line and phase currents for a balanced 3-phase delta-connected load. (8)
- b) Write the mathematical equations governing a 3-phase system. (2)

# 219A2

## PART II BASIC ELECTRONICS ENGINEERING

*Part II to be answered in pages 16 to 30*

### PART C

*(Answer all questions. Each question carries 4 marks)*

12. What is meant by avalanche breakdown?
13. Discuss about the principle of operation of a NPN transistor.
14. Explain about the concept of voltage divider biasing.
15. Discuss the working principle of a capacitor filter.
16. What is frequency reuse? Explain why hexagonal cell pattern is preferred over circular and square shapes.

### PART D

*(Answer one full question from each module, each question carries 10 marks)*

#### MODULE IV

17. a) Differentiate between Carbon composition resistor and Carbon film resistor (5)
- b) Discuss about the input-output characteristics of a BJT when connected in common emitter configuration. (5)

**OR**

18. a) Draw and explain the block diagram of a dc regulated supply. (5)
- b) Compare the characteristics of a half wave rectifier and full wave rectifier. (5)

#### MODULE V

19. a) With a neat diagram, illustrate the working of a RC coupled amplifier. (5)
- b) Discuss the role of coupling and bypass capacitors in single stage RC coupled amplifier. (5)

**OR**

20. a) Illustrate and explain the working of a PA system. (5)
- b) With a neat block diagram, discuss about an electronic instrumentation system. (5)

#### MODULE VI

21. a) Derive the expression for an amplitude modulated signal. (7)
- b) A modulating signal  $m(t)=10\cos(2\pi\times 10^3t)$  is amplitude modulated with a carrier signal  $c(t)=50\cos(2\pi\times 10^5t)$ . Calculate the modulation index and bandwidth. (3)

**OR**

22. Using neat diagrams, illustrate & explain the working of a (10)
  - a) Superheterodyne receiver.
  - b) Mobile communication system

\*\*\*\*\*