	4	12	5
U	I		อ

(Pages: 2)

Reg. No.....

Name.....

B.TECH. DEGREE EXAMINATION, MAY 2016

Sixth Semester

Branch: Applied Electronics and Instrumentation Engineering

AI 010 604—MICROCONTROLLER BASED SYSTEM DESIGN (AI)

(New Scheme—2010 Admission onwards)

[Regular/Improvement/Supplementary]

Time: Three Hours

Maximum: 100 Marks

Part A

Answer all questions.

Each question carries 3 marks.

- 1. Briefly explain the types of SPLDs.
- 2. Mention the features of 89C51 Microcontroller.
- 3. List and specify the specifications of ADC.
- 4. Describe 3-wire serial EEPROM.
- 5. Mention the features of a DS1302 real time clock.

LIBRARY E

 $(5 \times 3 = 15 \text{ marks})$

Part B

Answer all questions.

Each question carries 5 marks.

- 6. What are the advantages of a FPGA based system design?
- 7. Briefly explain memory organization in ARM processor.
- 8. Explain the working of successive approximation type ADC.
- 9. Compare RS 232, RS 422 and RS 482.
- 10. Briefly explain the LCD display with a neat sketch.

 $(5 \times 5 = 25 \text{ marks})$

Part C

Answer all questions.

Each full question carries 12 marks.

11. What is GAL? Explain 22 VID GAL with a neat sketch.

Or

12. Explain PAL operation with a neat sketch. Implement the function $X = A\overline{B}C + \overline{A}B\overline{C} + \overline{A}\overline{B} + AC$.

Turn over

13. Explain with a neat sketch the structure of ARM processor.

Or

- 14. With a neat block diagram, explain 89C2051. Mention its difference with 89C51.
- 15. Explain optically isolated TRIAC interface to 89C51 with a neat sketch. Write a C program for the same.

Or

- 16. Explain different types of DAC.
- 17. Explain 2-wire serial EEPROM interface with microcontroller with the help of necessary diagrams.

O

- 18. Explain the PCI bus interface with microcontroller. Write an assembly language program for the same.
- 19. Explain the interfacing of DIP switch with microcontroller.

Or

20. Explain how L293 motor driver is used with the microcontroller, with a neat circuit.

 $(5 \times 12 = 60 \text{ marks})$

