

Register No:

Name:

SAINTGITS COLLEGE OF ENGINEERING (AUTONOMOUS)

(AFFILIATED TO APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY, THIRUVANANTHAPURAM)


FRESHER ODD (SEMESTER 1) B.TECH DEGREE EXAMINATION (R), NOVEMBER 2024**Common to Computer Science and Engineering & Electrical and Electronics Engineering
(2024 SCHEME)****Course Code : 24EST1005-E****Course Name : Introduction to Electrical and Electronics Engineering****Max. Marks : 60****Duration: 2.5 Hours****PART I: ELECTRICAL ENGINEERING***Part I to be answered in pages 1 to 15***PART A***(Answer all questions. Each question carries 3 marks)*

1. State Kirchhoff's Current Law (KCL) and explain how it is used in circuit analysis.
2. What is reluctance in a magnetic circuit? Write its formula and explain the factors that affect the reluctance of a material.
3. A series circuit with $R = 10\Omega$ and $C = 50\mu F$ has an applied voltage with a frequency such that the current leads by 30° . What is the frequency of the voltage?
4. What are the advantages of three-phase systems over single-phase systems?

PART B*(Answer one full question from each module, each question carries 6 marks)***MODULE I**


5. Find the total resistance of the circuit between the points A and B.

6

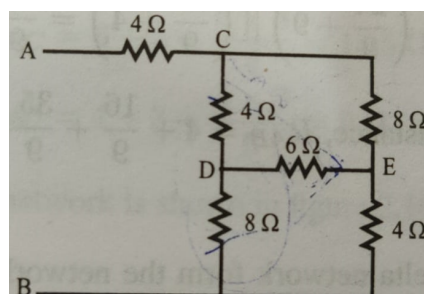**OR**

6. Determine the currents i_1 , i_2 and i_3 in the circuit shown below using mesh analysis.

6

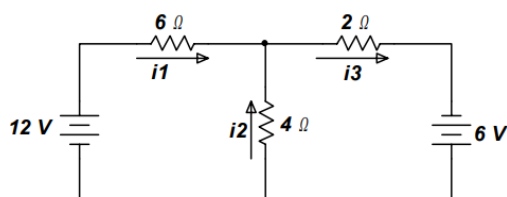

MODULE II

7. An iron ring of mean circumference 200cm is uniformly wound with 500 turns of wire. Calculate the value of flux density to produce a current of 1 A in the ring. 6
Assume $\mu_r = 1200$.

OR


8. A coil of 200 turns of wire is wound on a magnetic circuit of reluctance 2000AT/Wb. If a current of 1A flowing in the coil is reversed in 10ms, find the average emf induced in the coil. 6

MODULE III

9. With a phasor diagram, derive the instantaneous power equation, when alternating current is supplied through a series RL circuit. Also, draw the impedance triangle and write an expression for active, reactive, and apparent power in the RL circuit. 6

OR

10. Find the average and rms value of a full wave rectifier output voltage waveform. 6

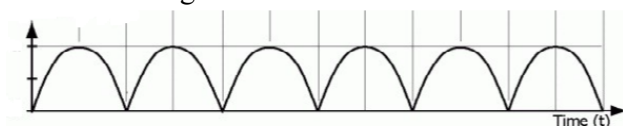

PART II: ELECTRONICS ENGINEERING

Part II to be answered in pages 16 to 30

PART A

(Answer all questions. Each question carries 3 marks)

11. A resistor has a color band sequence green, orange, red and gold. Find the terminal value and range of value which this resistor may have?
12. What is the purpose of filtering in a DC power supply?
13. What is the function of light sensors in instrumentation?
14. Describe the basic principle of operation of temperature sensors.

PART B

(Answer one full question from each module, each question carries 6 marks)

MODULE IV

15. Explain the input and output characteristics of a common emitter configuration, including their graphical representations. 6

OR

16. Differentiate zener and avalanche breakdown. 6

MODULE V

17. Compare the principles of amplitude modulation (AM) and frequency modulation (FM). 6

OR

18. Explain the block diagram of GSM architecture. 6

MODULE VI

19. Discuss the operation of solenoids and relays, and how they are used in switching applications. 6

OR

20. Explain the working principle of a load cell and its applications in weight measurement. 6
