

**R1908**

**Final Scheme/ Answer Key for Valuation**

*Scheme of evaluation (marks in brackets) and answers of problems/key*

**APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY**

FIRST SEMESTER B.TECH DEGREE EXAMINATION, DECEMBER 2018

**Course Code: BE101-04**

**Course Name: INTRODUCTION TO ELECTRONICS ENGINEERING**

Max. Marks: 100


Duration: 3 Hours

**PART A**

*Answer all questions, each carries 5 marks.*

Marks

- |   |  |     |
|---|--|-----|
| 1 | Specifications of a resistor (any four) -2 marks<br>Value of resistor and tolerance percentage- 680K $\Omega$ $\pm$ 5% --2 marks<br>The minimum and maximum resistance values -546 K $\Omega$ and 714 K $\Omega$ -1 mark | (5) |
| 2 | V-I characteristics of an ideal diode and piecewise linear model- 4 marks<br>Explanation-1 mark  | (5) |
| 3 | 3 different configurations with figure-3 marks (1 mark each)<br>Input resistance comparison-1 mark<br>output resistance comparison-1 mark  | (5) |
| 4 | 3 parameters of a JFET –3 marks(1 mark each)<br>Finding relation connecting JFET parameters-2 marks  | (5) |
| 5 | Circuit Diagram – 3 marks<br>Waveform- 2 marks   |     |

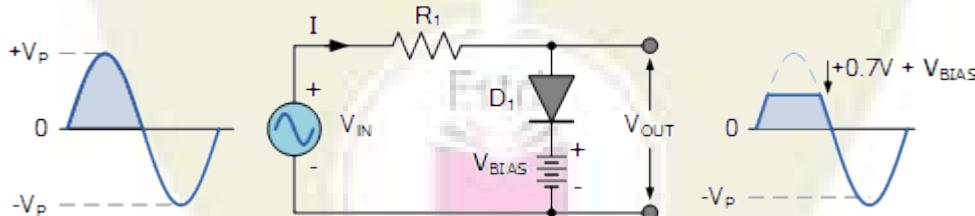

$$V_{BIAS} = 4.3V$$

Marks may be given if diode drop is not considered and take  $V_{BIAS} = 5V$

- |   |   |     |
|---|---|-----|
| 6 | Any five parameters of (1) Half Wave Rectifier- 2.5 marks<br>(2) Half Wave Rectifier- 2.5 marks | (5) |
| 7 | Diagram-3 marks<br>Working-2 marks  | (5) |

- 8 Accuracy- 1 mark  
Precision-2 mark (5)  
Resolution -2 marks

### PART B

*Answer six questions, one full question from each module and carries 10 marks.*

#### Module 1

- 9 Any four types with the dielectric and plate materials mentioned- 2 marks (10)  
Construction of any two(4 marks each)- 8 marks

**OR**

- 10 a) Any 3 classification-(1/2 mark each)-1.5 marks (6)  
Features(type of core) and uses of each-(1.5 marks each)-4.5 marks  
b) Operating principle(2 marks) (4)  
Classification(2 marks)

#### Module 1I

- 11 a) Explanation –Zener break down - 2.5 marks (5)  
Avalanche breakdown- 2.5 marks  
b) What is doping-2 mark (5)  
Mechanism of current flow in a P type semiconductor- 3 marks

**OR**

- 12 (a) Solar cell  
Diagram -2 marks, Explanation-3 marks (10)  
(b) Photo diode  
Diagram -2 marks, Explanation-3 marks

#### Module 1II

- 13 a) Diagram-2marks (5)  
Explanation-3 marks  
b) Define the parameters  $\beta$  and  $\alpha$  (1 each)- 2 marks (5)  
Derivation of the relation -3 marks

**OR**

- 14 a) Circuit diagram -3 marks (6)  
Explanation of different components-3 marks

b) Equations-

$$I_c = \beta I_B, \alpha = \beta/(1+\beta) \quad -1 \text{ mark}$$

The value of  $\alpha_{dc}$  - 1.5 marks

New value of  $I_C$  - 1.5 marks

(4)

$$\text{Ans: } \alpha_{dc} = 0.99$$

$$\text{New } I_c = 1 \text{ mA}$$

### Module 1V

15 Sketch -3 marks

Explanation-4 marks

(10)

Drain characteristics with explanation-3 marks

**OR**

16 a) Equivalent circuit of UJT-2 marks

Explanation-2 marks

(6)

Intrinsic stand-off ratio-2 marks

b) Any four comparisons-(1 mark each)- 4marks

(4)

### Module V



17 a) Positive clamping circuit diagram -2 marks

(4)

Explanation -2 marks

b) Circuit -3 marks

Input and output waveforms- 3 marks

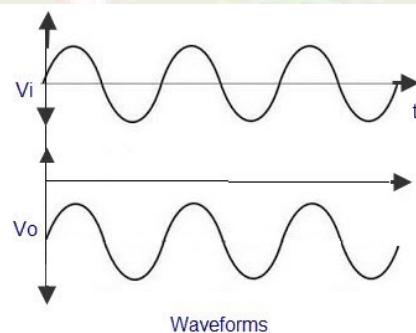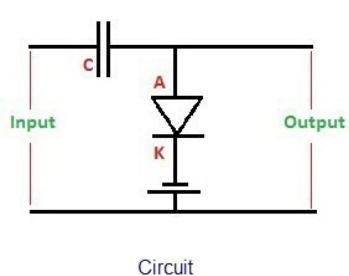

(6)

$V_i$  between -5V and +5V

$V_o$  between -15 and -5V

Voltage source is -3.7 V (-3V if diode drop neglected)

**OR**

18 Block diagram of a DC power supply-4 marks

(10)

Explanation of each block - 6 marks

## **Module VI**

- 19 a) Block diagram of CRO -3 marks (6)  
Explanation the functions of each block-3 marks  
b) Measurement voltage and frequency-(2 each)-4 marks (4)

**OR**

- 20 Block diagram-4 marks (10)  
Measurement of voltage, current and resistance-(2 marks each)-6 marks

