

Reg No.: \_\_\_\_\_

Name: \_\_\_\_\_

**APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY**  
THIRD SEMESTER B.TECH DEGREE EXAMINATION, DECEMBER 2018

**Course Code: EC201**

**Course Name: NETWORK THEORY**

Max. Marks: 100


Duration: 3 Hours

**PART A**


*Answer any two full questions, each carries 15 marks.*

Marks

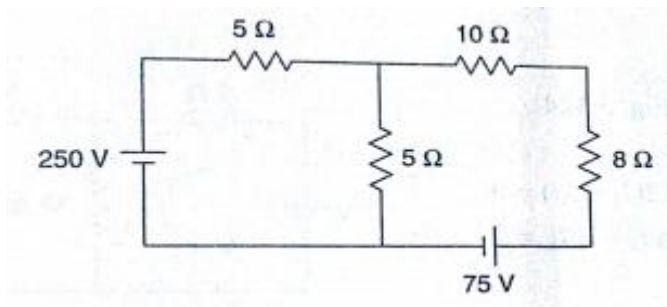
- 1 a) State and prove initial value theorem and final value theorem (8)  
 b) Find the current through  $8\ \Omega$  resistor in the network using Thevenin's theorem (7)



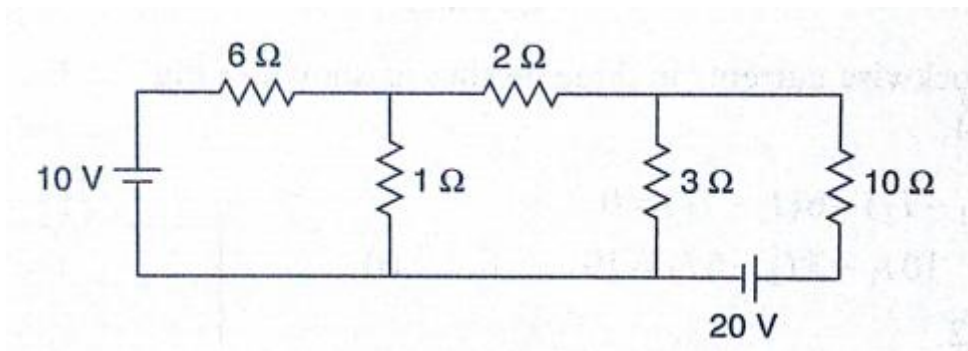- 2 a) Find the current through  $2\ \Omega$  resistor using Mesh analysis (8)



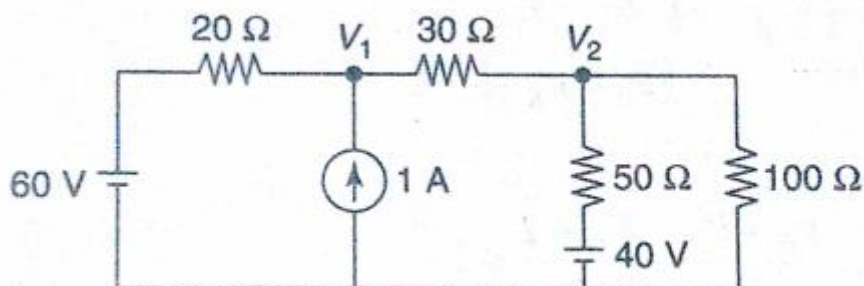
- b) Find the current in the  $100\ \Omega$  resistor using Nodal analysis (7)



- 3 a) State and prove maximum power transfer theorem when the load impedance is a (8)

complex impedance with variable resistance and variable reactance

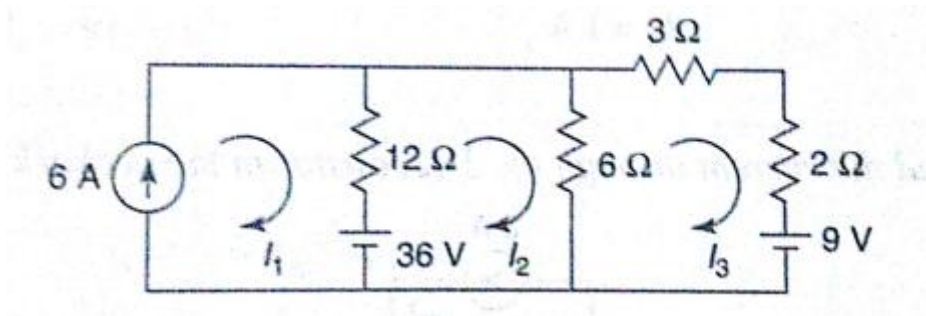- b) Find the current through the  $2\ \Omega$  resistor (7)




**PART B**


*Answer any two full questions, each carries 15 marks.*

- 4 a) Solve  $\frac{dy}{dt} + 2y = e^{-3t}$ ,  $y(0) = 1$  (8)

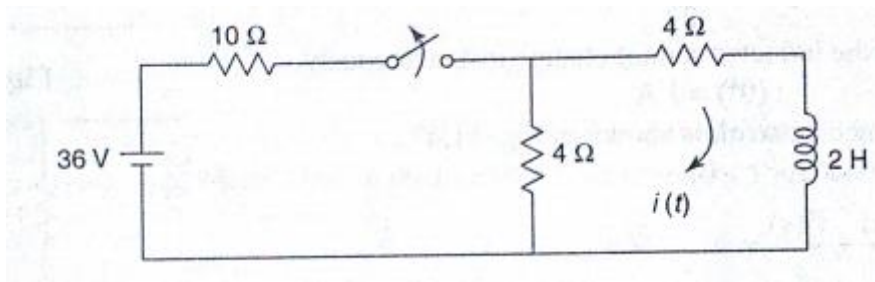
- b) The network shown has acquired steady state with the switch closed for  $t < 0$ . At  $t = 0$ , the switch is opened. Obtain  $i(t)$  for  $t > 0$ . (7)



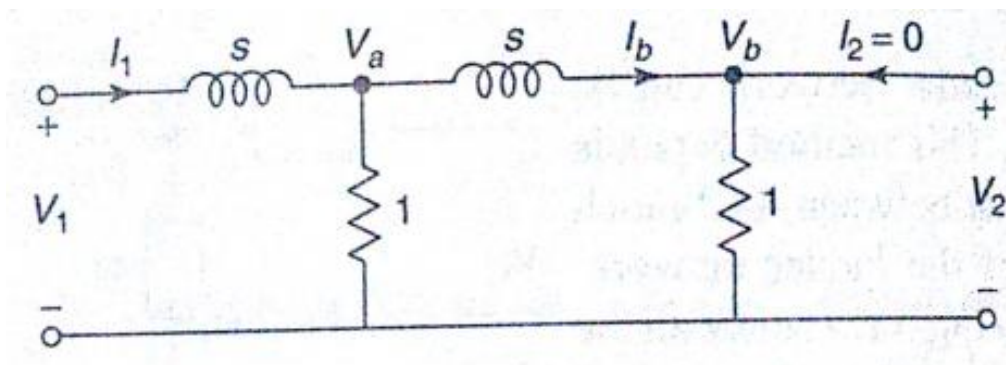
- 5 a) For the network determine the voltage transfer function  $V_2/V_1$  (7)



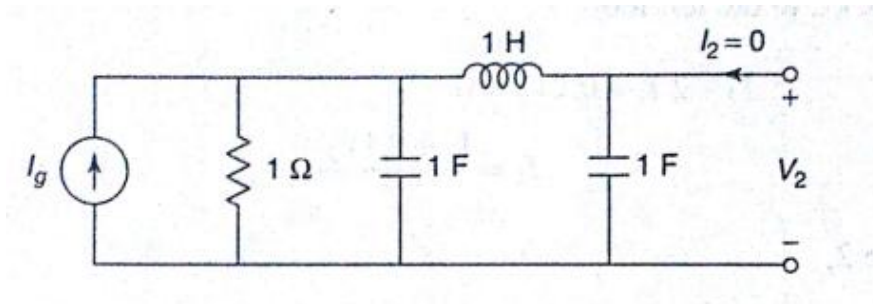
- b) For the network shown determine  $V_2/I_g$ . Plot the pole zero diagram of  $V_2/I_g$ . (8)



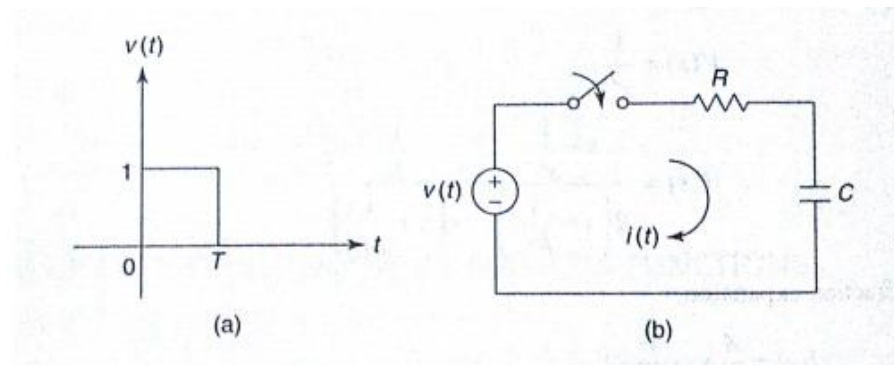- 6 a) A rectangular voltage pulse of unit height and  $T$  second duration is applied to a series RC network at  $t=0$ . Obtain the expression for current  $i(t)$ . Assume the capacitor to be initially uncharged. (7)



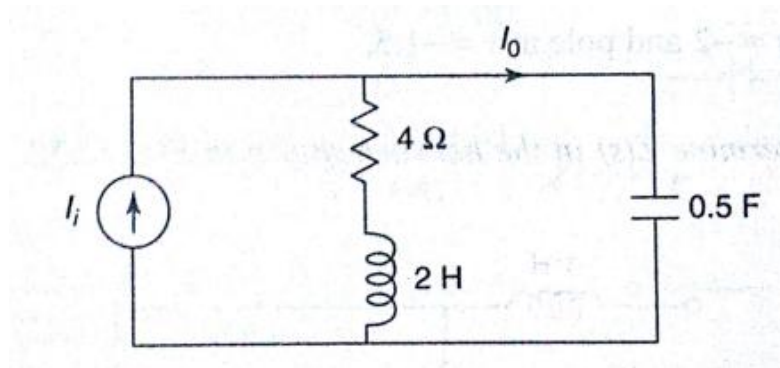
- b) For the network shown plot poles and zeros of function  $I_0/I_i$  (8)



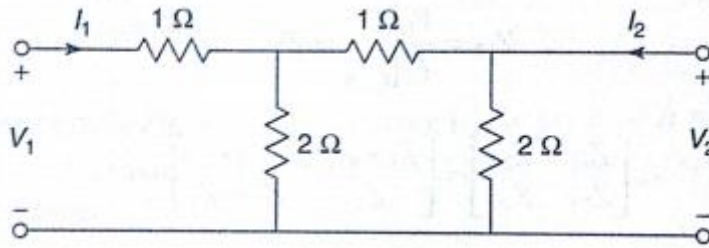
## PART C

Answer any two full questions, each carries 20 marks.

- 7 a) Find Z parameters for the network shown (10)



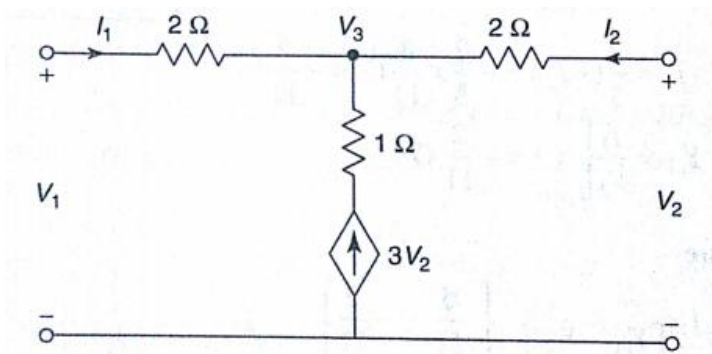- b) Find the Y parameters of the network shown (10)



- 8 a) Derive the resonance frequency for a series RLC circuit and give its power factor, current and voltage at resonance (10)
- b) A series RLC circuit has a quality factor of 5 at 50 rad/s. The current flowing through the circuit at resonance is 10 A and the supply voltage is 100 V. Find the circuit constants R,L and C (10)
- 9 a) Compare series and parallel resonant circuits (current, impedance, power factor, resonant frequency and Q factor) (10)
- b) A coil of 10  $\Omega$  resistance and 2 H inductance is connected in parallel with a variable capacitor across a 220 V, 50 Hz supply. Calculate (a) the capacitance of the capacitor for the resonance, (b)the dynamic impedance of the circuit and (c) supply current (10)

\*\*\*\*\*