



## Scheme of Valuation/Answer Key

**APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY**  
**THIRD SEMESTER B.TECH DEGREE EXAMINATION, DECEMBER 2018**

**Course Code: EE201**

**Course Name: CIRCUITS AND NETWORKS**

Max. Marks: 100

Duration: 3 Hours

### PART A


*Answer all questions, each carries 5 marks.*

			Marks
1		$I = \frac{23}{12} = 1.9A$ ( by any method) ..... 5 marks	(5)
2		Directed Graph .... 5 marks  <div style="text-align: center;"> </div>	(5)
3		$v_c = V(1 - e^{-t/RC})$ $50 = 100(1 - e^{-5/RC})$ $R = 1.44 \times 10^6 \Omega$ ..... 5 marks	(5)
4		$(Ls + R)I(s) = \frac{50}{s} Li(0)$ $i(t) = 10 - 8e^{-2000t}$ A ..... 5 marks	(5)
5		$Z_{21}(s) = \frac{1}{2s}$ ..... 2 ½ marks $Y_{11}(s) = \frac{2s}{10s^2 + 1}$ ..... 2 ½ marks	5
6		Derivation ..... 5 marks	5
7		Differences .... 5 marks	5
8		Not Hurwitz .... 1 mark Continued expansion & proof .... 4 marks (or find roots)	5

### PART B

*Answer any twofull questions, each carries 10 marks.*

9		$I = \frac{50 \angle 90^\circ}{3 + j4} = 10 \angle 53.13^\circ$ ..... 10 marks	(10)
10		Draw oriented graph .... 2 marks Tie set matrix .... 2 marks Branch impedance matrix ..... 1 mark Voltage source matrix ..... 1 mark Current source matrix ..... 1 mark	(10)

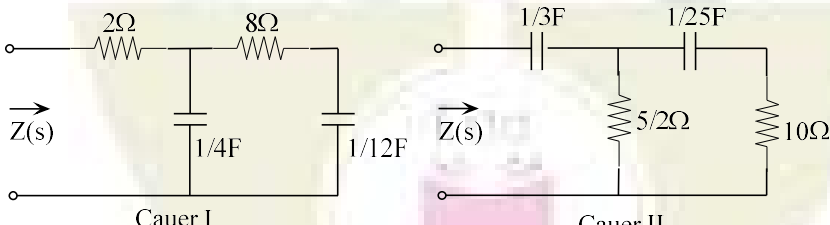	$\begin{bmatrix} 20 \\ -50 \\ 0 \end{bmatrix} = \begin{bmatrix} 14-j4 & -10 & j4 \\ -10 & 20+j5 & -j5 \\ j4 & -j5 & 3+j \end{bmatrix} \begin{bmatrix} I_{11} \\ I_{12} \\ I_{13} \end{bmatrix} \dots\dots 3 \text{ marks (solution not essential)}$	
11	$Z_N = 0.01\Omega \dots\dots 3 \text{ marks}$ $I_N = 9659.3\angle 15^\circ A \dots\dots 3 \text{ marks}$ $I = 30.52\angle -56.4^\circ A \dots\dots 4 \text{ marks}$	10
<b>PART C</b>		
<i>Answer any twofullquestions, each carries10 marks.</i>		
12	$v_c(0) = 200V \dots\dots 2 \text{ marks}$ $i(t) = -10e^{-2500t} A \dots\dots 8 \text{ marks}$	(10)
13	$v_c(0) = 1V; i_L(0) = 1A \dots\dots 3 \text{ marks}$ $0.5\frac{di}{dt} + i + \frac{1}{C} \int_{-\infty}^t idt = 0 \dots\dots 2 \text{ marks}$ $I(s) = \frac{3s}{(s+1)^2 + 1} \dots\dots 3 \text{ marks}$ $i(t) = 3e^{-t}(\cos t - \sin t) \dots\dots 2 \text{ marks}$	(10)
14	$i(0) = 2A \dots\dots 2 \text{ marks}$ $0.01\frac{di}{dt} + 25i = 100 \dots\dots 4 \text{ marks}$ $i(t) = 4 - 2e^{-2500t} A \dots\dots 4 \text{ marks}$	
<b>PART D</b>		
<i>Answer any twofull questions, each carries 10 marks.</i>		
15	$Y = \begin{bmatrix} 1.5 & -0.5 \\ -0.5 & 1.5 \end{bmatrix} \dots\dots 5 \text{ marks}$ $Z = \begin{bmatrix} 0.75 & 0.25 \\ 0.25 & 0.75 \end{bmatrix} \dots\dots 5 \text{ marks}$	(10)
16	 <p>Cauer I ..... 5 marks    Cauer II ..... 5 marks</p>	(10)
17	$Z(s) = 2 + \frac{4s+6}{s(s+2)} = 2 + \frac{3}{s} + \frac{1}{s+2} \dots\dots 2 \text{ marks}$ Foster I form ..... 3 marks $\frac{Y(s)}{s} = \frac{1/4}{s+1} + \frac{1/4}{s+3} \dots\dots 2 \text{ marks}$ Foster II form ..... 3 marks	10

