



Scheme of Valuation/Answer Key

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY
THIRD SEMESTER B.TECH DEGREE EXAMINATION, JUNE 2019

Course Code: EC201

Course Name: NETWORK THEORY

Max. Marks: 100

Duration: 3 Hours

PART A

Answer any two full questions, each carries 15 marks.

Marks

- 1 a) Mesh equations (6) Current through 10Ω (1) Voltage across 10Ω (1) (8)
- $$(7 + j3)I_1 - j5I_2 - 5I_3 = 10$$
- $$-j5I_1 + (12 + j3)5I_2 - (2 - j2)I_3 = -(4.33 + j2.5)$$
- $$-5I_1 - (2 - j2)I_2 + (17 - j2)I_3 = 0$$
- Current through 10Ω , $I_3 = 0.435 \angle -194.15^\circ$ A
Voltage across $10\Omega = 10I_3 = 4.35 \angle -194.15^\circ$ A
- b) Each property – 3.5 (statement-1, proof -2.5) (7)
- 2 a) Node equations (4) node voltages calculation (3) Current I (1) (8)
- $$V_1 = 24.763 \angle -287.74^\circ \text{ V} \quad V_2 = 34.3406 \angle -307.184^\circ \text{ V}$$
- $$I = -3.434 \angle 15.95^\circ \text{ A}$$
- b) Necessary equations and calculations (3+3) Voltage V_2 (1) (7)
- $$V_a = 12 \angle 53.14^\circ \text{ V} \quad V_b = 0.707V_2 \angle -45^\circ \text{ V}$$
- $$V_a = V_b \quad V_2 = 16.9731 \angle 98.14^\circ \text{ V}$$
- 3 a) Current/voltage through 10Ω with each source acting alone (2.5+2.5+2.5) (9)
- Calculation of voltage across 10Ω (1.5)
- 10 V source alone $I' = 0.44 \text{ A} (\rightarrow)$
- 2A source alone $I'' = 1.11 \text{ A} (\rightarrow)$
- 10V source alone $I''' = 0.55 \text{ A} (\leftarrow)$
- Current through $10\Omega = 1 \text{ A} (\rightarrow)$ Voltage across $10\Omega = 10 \text{ V}$

- b) Thevenin's voltage (3) Thevenin's resistance (2) Power dissipated (1) (6)
 $V_{Th} = 93.5V$ $R_{Th} = 22.75 \Omega$ $I = 2A$ Power = 96W

PART B

Answer any two full questions, each carries 15 marks.

- 4 a) Circuit (1) Necessary Equations (5) (6)
 b) Formulation of equation in terms of 's' (3) Partial Fraction Expansion (4) (9)
 Solution (2)

$$v(t) = \frac{1}{4} (1 + 2e^{-2t} + e^{-4t})u(t)$$

- 5 a) Pole – zero plot (2) Obtaining time domain response from plot (6) (8)

$$V(s) = \frac{3}{s+2} + \frac{2}{s+7} \quad v(t) = 3e^{-2t} + 2e^{-7t}$$

- b) Initial current (2) Calculation of current (5) (7)

$$i(0^-) = 3.33 A \quad i(t) = 5 - 1.667e^{-200t} A$$

- 6 a) Necessary conditions (6) (6)
 b) Calculations of each parameter (2+2+2) Values (1+1+1) (9)

$$\frac{I_2(s)}{I_1(s)} = \frac{1}{4s^2 + 4s + 1}$$

$$\frac{V_2(s)}{V_1(s)} = \frac{1}{4s^3 + 4s^2 + 2s + 1}$$

$$\frac{V_1(s)}{I_1(s)} = \frac{8s^3 + 8s^2 + 4s + 2}{4s^2 + 4s + 1}$$

PART C

Answer any two full questions, each carries 20 marks.

- 7 a) Circuit diagram (2) Derivation (4) (6)
 b) Equations and calculations (5) Each parameter (1+1+1+1) (9)

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} s^4 + 3s^2 + 1 & \frac{(s^4 + 3s^2 + 1)^2 - 1}{s(s^2 + 2)} \\ s(s^2 + 2) & s^4 + 3s^2 + 1 \end{bmatrix}$$

- c) Definitions (2.5+2.5) (5)
 8 a) Equations and calculations (4) Values of R, L and C (1+1+1) Maximum current (10)
 (1) Half power frequencies (2)

$$R=33.33\Omega \quad L=7.08mH \quad C=1.56mF$$

b) Equations (6) Each parameter (1+1+1+1) $[Z] = \begin{bmatrix} 7 & 1 \\ 2 & 2 \\ 1 & 7 \\ 2 & 2 \end{bmatrix}$ (8)

9 a) Circuit diagram (2) Steps involved (6) maximum output voltage (2) maximum amplification factor (2) (12)

b) Equations and calculations (6) Drop across the capacitor (2) (8)

$$I_1 = 0.06324 \angle -42.83^\circ \text{A} \quad I_2 = 0.5059 \angle -42.82^\circ \text{A}$$

$$\text{Drop across the capacitor} = 3.0354 \angle -132.82^\circ \text{V}$$

