

Reg No.: _____

Name: _____

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY
SIXTH SEMESTER B.TECH DEGREE EXAMINATION(S), DECEMBER 2019

Course Code: AE312
Course Name: POWER ELECTRONICS

Max. Marks: 100

Duration: 3 Hours

PART A

Answer any two full questions, each carries 15 marks.

		Marks
1	a) Draw the structure of Power diode and explain its operating principle.	10
	b) What is reverse recovery time of a diode?	5
2	a) With two transistor analogy explain the characteristics of SCR.	10
	b) Explain safe operating area of Power BJT.	5
3	Explain the working of single phase fully controlled bridge rectifier with RL load. Draw relevant waveforms.	15

PART B

Answer any two full questions, each carries 15 marks.

4	a) Explain the principle of operation of chopper.	5
	b) Describe the principle of step-up chopper. Derive the expression for the average output voltage in terms of input voltage and duty cycle.	10
5	a) With circuit diagram explain the operation of full bridge inverter	10
	b) Draw the circuit diagram of single phase McMurray-Bedford full bridge inverter	5
6	Write short notes on (1) voltage control of inverters (2) current source inverters (3) vector control of induction motors	15

PART C

Answer any two full questions, each carries 20 marks.

7	a) Describe ON line and OFF line UPS.	10
	b) List various types of SMPS. Describe SMPS with Push-Pull configuration.	10
8	a) Explain the drive requirements of Power BJT.	10
	b) With circuit diagram, explain any two base drive circuits for Power MOSFET.	10
9	Explain the methods for control of power electronic circuits using microprocessors and microcontrollers.	20
