

Reg No.: \_\_\_\_\_

Name: \_\_\_\_\_

**APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY**  
**SIXTH SEMESTER B.TECH DEGREE EXAMINATION(R&S), MAY 2019**

**Course Code: EE364**

**Course Name: SWITCHED MODE POWER CONVERTERS**

Max. Marks: 100

Duration: 3 Hours

*Graph Sheets will be provided*

**PART A**

*Answer all questions, each carries 5 marks.*

Marks

- |   |   |     |
|---|---|-----|
| 1 | Obtain the input-output voltage and current relation as a function of duty ratio for a Boost dc-dc converter in continuous conduction mode. | (5) |
| 2 | What is linear power supply? Mention the drawbacks of linear power supply.  | (5) |
| 3 | Explain the basic concept of a push pull converter derived from buck converter.   | (5) |
| 4 | Define the terms amplitude modulation ratio and frequency modulation ratio in a PWM switching scheme.                                       | (5) |
| 5 | Compare PWM technique and space vector modulation technique.  | (5) |
| 6 | Explain the concept of tolerance band current control technique.  | (5) |
| 7 | What is meant by resonant converters? How are they useful in SMPC applications?   | (5) |
| 8 | Briefly explain the characteristics of an undamped series resonant circuit.   | (5) |

**PART B**

*Answer any two full questions, each carries 10 marks.*

- |    |   |     |
|----|---|-----|
| 9  | a) For an ideal buck converter, derive the value for $L_{crit}$ in terms of duty cycle, switching frequency, and load at the boundary of discontinuous conduction mode (DCM) and continuous conduction mode (CCM).                                  | (5) |
|    | b) In a step up converter, consider all components to be ideal. Let $V_d$ be 8-16 V, $V_o = 24V$ , $f_s = 20kHz$ , and $C = 470\mu F$ . Calculate $L_{min}$ that will keep the converter operating in continuous conduction mode if $P_0 \geq 5W$ . | (5) |
| 10 | a) With help of neat sketches derive the expression for the voltage ripple in an ideal buck-boost converter.  | (5) |

- b) In a Cuk converter shown in Figure 1, operating at 50 kHz,  $L_1 = L_2 = 1$  mH and  $C_1 = 5$   $\mu$ F. The capacitor is sufficiently large to yield an essentially constant output voltage. Here,  $V_d = 10$  V and the output  $V_o$  is regulated to be constant at 5V. It is supplying 5 W to a load. Assume ideal conditions. Calculate the RMS current flowing through the capacitor  $C_1$  (5)

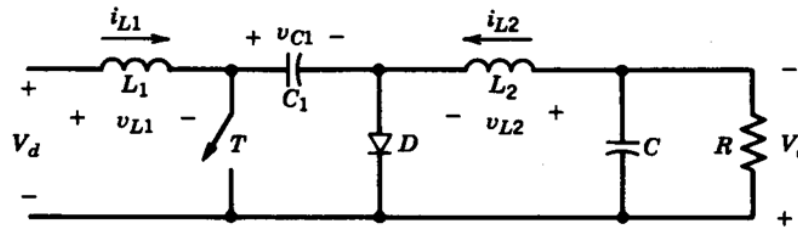


Figure 1

- 11 a) With help of neat sketches explain the operation of full bridge DC-DC converter with bipolar voltage switching scheme. (6)
- b) Write a short note on the electrical isolation in DC-DC converters. (4)

### PART C

*Answer any two full questions, each carries 10 marks.*

- 12 a) With help of neat sketches explain the operation of a flyback converter (6)
- b) A forward converter with a demagnetising winding is designed to operate with a maximum duty ratio  $D_{max}$  of 0.7. Calculate the voltage rating of the switch in terms of input voltage  $V_d$ . (4)
- 13 a) With help of relevant sketches explain the operation of a full bridge DC power supply. (5)
- b) Explain the control of a single phase full bridge inverter with PWM unipolar voltage switching scheme. (5)
- 14 a) How the output voltage of a single phase inverter is controlled using voltage cancellation technique? Explain. (5)
- b) Explain the operation of a three phase inverter with square wave switching scheme. (5)

### PART D

*Answer any two full questions, each carries 10 marks.*

- 15 a) Explain the concept of space vector and space vector modulation technique. (5)
- b) Explain the concept of programmed harmonic elimination switching scheme to (5)

control the inverter output.

- 16 a) Write a short note on the current mode control of inverters (3)
- b) Explain the operation of a ZCS resonant converter with necessary figures and circuit diagram. (7)
- 17 a) With help of neat circuit diagram and relevant waveforms, discuss the operation of series loaded resonant dc-dc converter in discontinuous current conduction mode. (7)
- b) Compare zero voltage switching (ZVS) and zero current switching(ZCS) (3)