

Register No.: Name:

SAINTGITS COLLEGE OF ENGINEERING (AUTONOMOUS)

(AFFILIATED TO APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY, THIRUVANANTHAPURAM)

SECOND SEMESTER B.TECH DEGREE EXAMINATION (Special), AUGUST 2021

Course Code: 20EST130

Course Name: Basics of Electrical and Electronics Engineering

Max. Marks: 100

Duration: 3 Hours


PART I BASIC ELECTRICAL ENGINEERING*Part I to be answered in pages 1 to 15***PART A***(Answer all questions. Each question carries 4 marks)*

CO

1. A 50 Ω resistor is in parallel with a 100 Ω resistor. Current in 100 Ω is 3.6 A. What is the value of third resistance to be added in parallel to this circuit to make the total current 12.1 A? [1]
2. State and explain Faraday's Laws of electromagnetic induction. [2]
3. Define the terms (i) Peak factor and (ii) Form factor for a fully rectified sine wave. [3]
4. Derive the relation between line current and phase current in a three-phase star connected system. [3]
5. A 100 Ω resistor in series with 150 μF capacitor is connected to 230 V, 50 Hz supply. Find i) impedance ii) current iii) power factor iv) voltage across the resistor [3]


PART B*(Answer one full question from each module, each question carries 10 marks)***MODULE I**

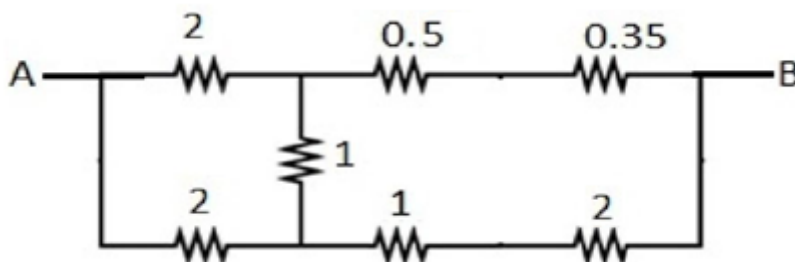6. a) State and explain Kirchoff's laws with examples. [1] (4)
- b) Determine the equivalent resistance across the terminals A and B. All resistors are given in ohms. [1] (6)



OR


- | | | CO | Marks |
|----|---|-----------|--------------|
| 7. | a) What are the steps to be followed in nodal analysis? | [1] | (3) |
| | b) Calculate the current flowing through $30\ \Omega$ and $50\ \Omega$ resistors using mesh analysis for the following circuit. | | |

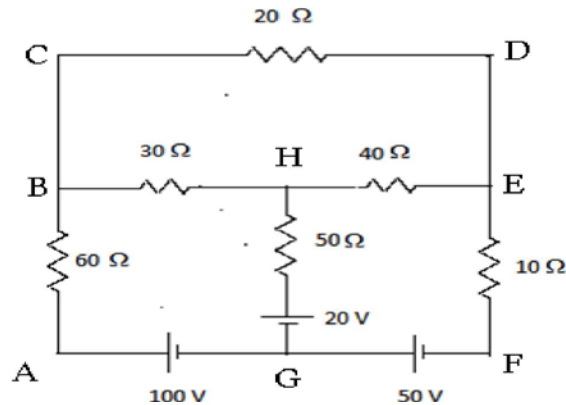

[1] (7)

MODULE II

- | | | CO | Marks |
|----|---|-----------|--------------|
| 8. | a) A mutual inductor with co-efficient of coupling equal to one is made from a primary coil of inductance 10 mH and a secondary coil of 20 mH. Find the value of mutual inductance. | [2] | (3) |
| | b) Determine the effective and mean value of the given voltage waveform. | | |

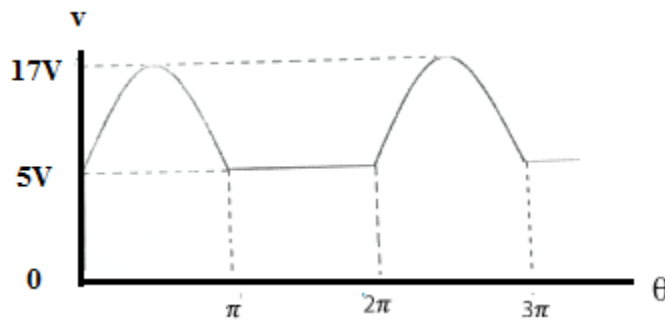

[2] (7)

OR

- | | | CO | Marks |
|----|--|-----------|--------------|
| 9. | A steel ring of 25 cm diameter and of circular section 3 cm in diameter has an air gap of 1.5 mm length. It is uniformly wound with 1000 turns of wire carrying a current of 2 A. Calculate i) magneto motive force ii) magnetic flux density in air gap iii) magnetic flux iv) relative permeability of steel ring. Assume that iron path takes about 40% of the total mmf. | [2] | (10) |

MODULE III

- | | | CO | Marks |
|-----|---|-----------|--------------|
| 10. | a) Prove that the total power consumed by a purely inductive circuit is zero. | [3] | (4) |
| | b) Determine for a series RLC circuit with $R = 15\ \Omega$, $L = 2\ \text{mH}$, $C = 1\ \mu\text{F}$:
(i) Impedance (ii) Current (iii) Voltage across L and C (iv) Power delivered to R (v) Power factor. The circuit is connected to a voltage source of voltage $v = 50 \sin 628t$. | [3] | (6) |

OR

- | | CO | Marks |
|---|-----------|--------------|
| 11. Three inductive coils, each with a resistance of 22Ω and an inductance of 0.05 H are connected in (i) star and (ii) delta, to a three phase 415 V , 50 Hz supply. Calculate for each of the above cases (i) phase current and line current and (ii) total power absorbed. | [3] | (10) |

PART II BASIC ELECTRONICS ENGINEERING

Part II to be answered in pages 16 to 30

PART A

(Answer all questions. Each question carries 4 marks)

- | | CO | |
|--|-----------|-----|
| 12. For the samples given below, specify the nominal value, tolerance, maximum and minimum value | | |
| a) A resistor coloured – yellow, violet, orange and gold | | [4] |
| b) A capacitor with code 104K | | |
| 13. Differentiate between avalanche breakdown and zener breakdown. | | [4] |
| 14. Draw the block diagram of DC power supply and specify the functions of each block. | | [5] |
| 15. Explain voltage divider biasing. | | [5] |
| 16. Illustrate the concept of frequency reuse in cellular communication. | | [6] |

PART B

(Answer one full question from each module, each question carries 10 marks)

MODULE IV

- | | CO | Marks |
|---|-----------|--------------|
| 17. a) Explain the specifications and features of carbon composition type resistors and carbon film type resistors. | [4] | (5) |
| b) With necessary diagrams and waveforms, describe the V-I characteristics of a PN junction diode. | [4] | (5) |

OR

- | | CO | Marks |
|--|-----------|--------------|
| 18. a) Draw and outline the input and output characteristics of common emitter transistor configuration. | [4] | (6) |
| b) Obtain the relation between the current gains β and α | [4] | (4) |

MODULE V

- | | CO | Marks |
|---|-----------|--------------|
| 19. With necessary diagrams and waveforms, explain the working of a full wave bridge rectifier with capacitor filter. | [5] | (10) |

OR

	CO	Marks
20. With circuit diagram and waveforms, explain the working of a common emitter RC coupled amplifier. Draw and explain its frequency response.	[5]	(10)

MODULE VI

	CO	Marks
21. a) List about the frequency bands used for various communication systems.	[6]	(4)
b) With the help of block diagram, outline the working of super heterodyne receiver.	[6]	(6)

OR

	CO	Marks
22. a) Describe the principle of operation of GSM with block diagram	[6]	(6)
b) What is modulation. Differentiate between amplitude modulation and frequency modulation.	[6]	(4)
