

Register No.: Name:

SAINTGITS COLLEGE OF ENGINEERING (AUTONOMOUS)

(AFFILIATED TO APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY, THIRUVANANTHAPURAM)

THIRD SEMESTER B.TECH DEGREE EXAMINATION (Regular), FEBRUARY 2022

**ELECTRICAL AND ELECTRONICS ENGINEERING
(2020 SCHEME)**

Course Code: 20EET201

Course Name: Circuits and Networks


Max. Marks: 100

Duration: 3 Hours

PART A

(Answer all questions. Each question carries 3 marks)

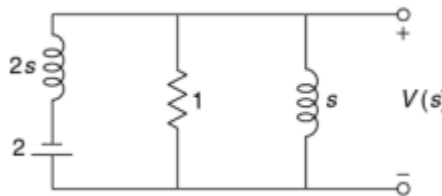1. State and explain Superposition theorem with suitable example.
2. State maximum power transfer theorem with its conditions and also derive equation for maximum power.
3. Obtain the time constant of a RL series circuit.
4. Obtain the expression for $V(s)$ in the following network.




5. Define Transfer function. Explain the concept of poles and zeros in transfer function.
6. Explain the importance of coefficient of coupling in a magnetic circuit.
7. A balanced delta connected load of impedance $(8-j6) \Omega$ per phase is connected to a three phase, 230V, 50Hz supply. Calculate a) power factor b) line current.
8. Derive the equations of phase currents in an unbalanced delta connected load.
9. Write the conditions for a two-port network to be symmetrical in case of all parameters.
10. Draw two port π network and write the corresponding parameter representations.

PART B

(Answer one full question from each module, each question carries 14 marks)

MODULE I

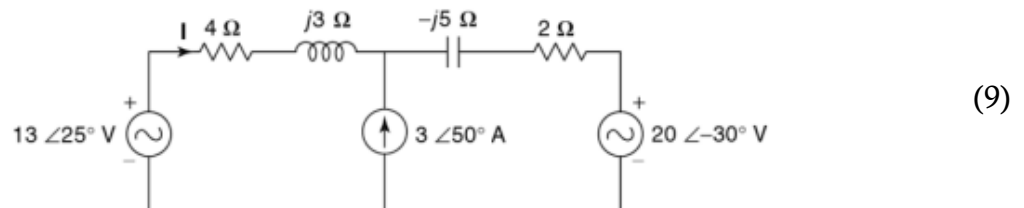
11. a) Find the current I in given network by superposition principle.




- b) Distinguish between Thevenin's and Norton's theorems (5)

OR

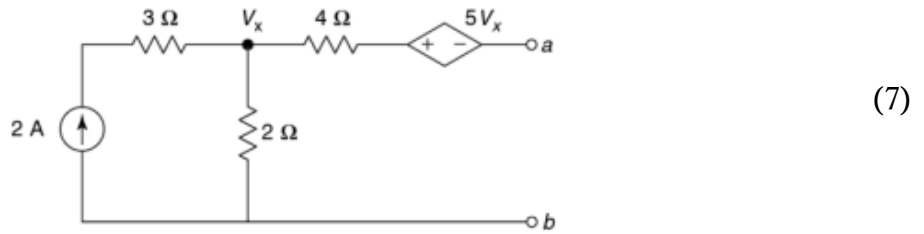12. a) Obtain the Thevenin's equivalent network for the given network diagram.




- b) Find the Norton's equivalent to the left of the terminals A-B for the network given.

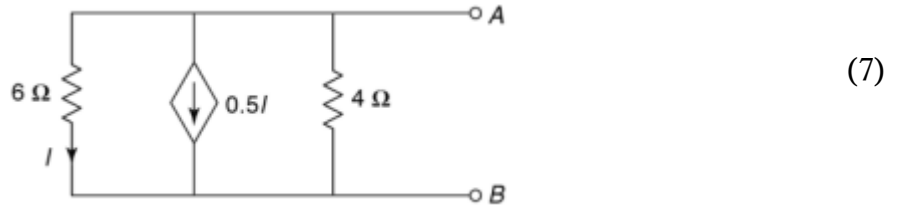


MODULE II

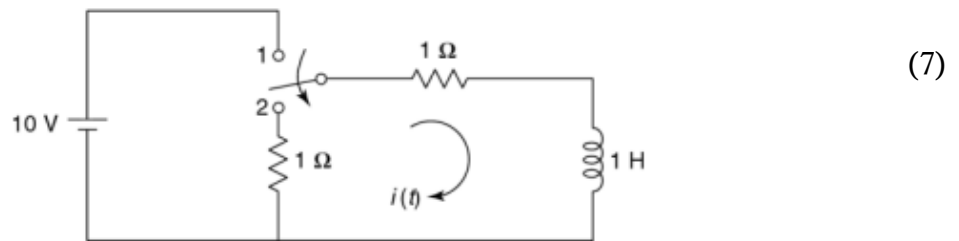13. a) In the network given below, the switch is moved from position 1 to 2 at $t = 0$, steady state condition having been established in the position 1. Determine $i(t)$ for $t > 0$.




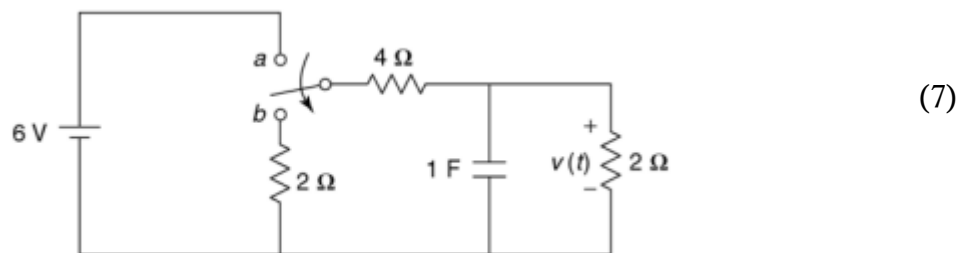- b) In the network given below, the switch is moved from position a to b at $t = 0$. Find $v(t)$.




OR

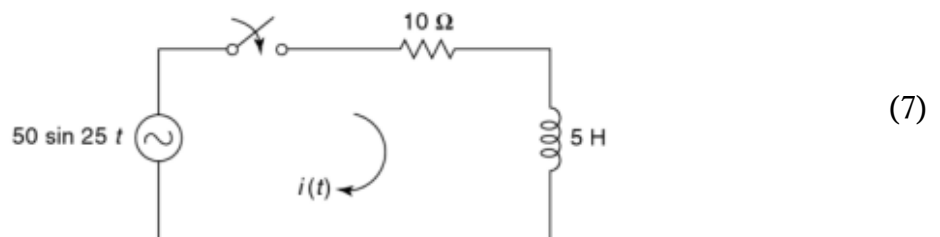14. a) Determine the current $i(t)$ in the network given when the switch is closed at $t = 0$.




- b) The switch in the given circuit is opened at time $t = 0$. Determine the voltage $v(t)$ for $t > 0$.
- (7)

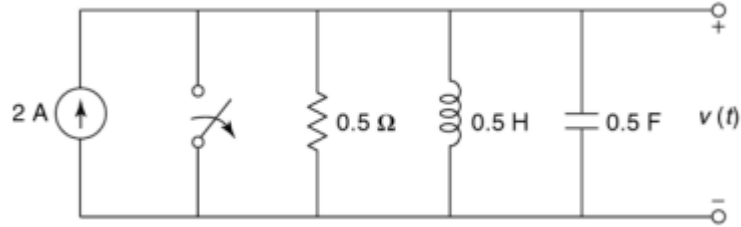


MODULE III

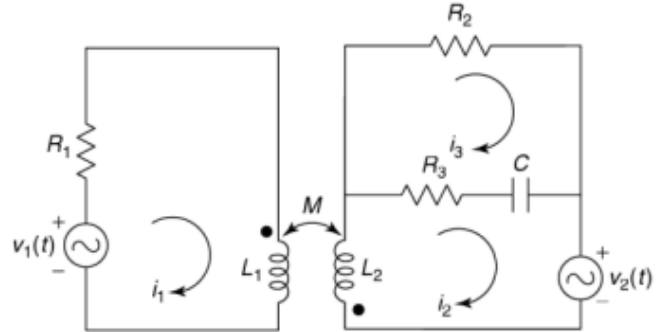15. a) Write the KVL equations for the circuit given below.



(7)

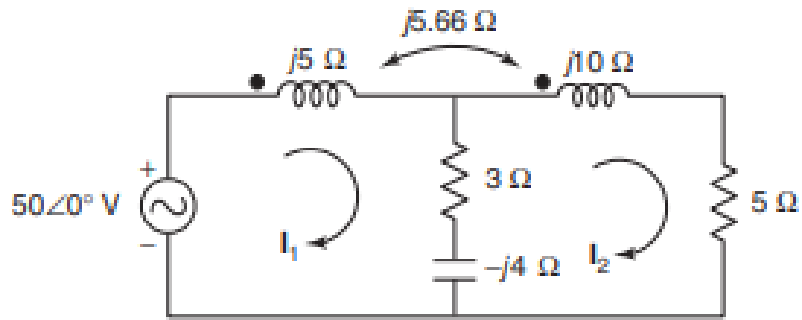
b) Write the mesh equations for network given below and solve I_1 and I_2



(7)

OR

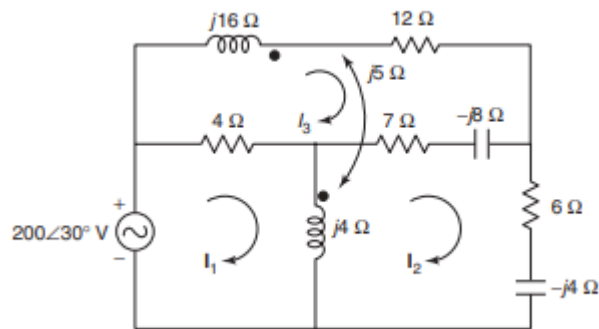16. a) Write the KVL equations for the circuit given below.



(9)

- b) Narrate the concept of dot convention in coupled circuits with an example. (5)

MODULE IV


17. a) A resistor and a capacitor are connected in series with a variable inductor. When the circuit is connected to a 230V, 50Hz supply, the maximum current obtained by varying the inductance is 2A. The voltage across the capacitor is 500V. Calculate the resistance, inductance and capacitance of the circuit. (5)
- b) A three phase 400V 4-wire system given below has a star connected load with $Z_a = (10+j0)\Omega$, $Z_b = (15+j10)\Omega$, $Z_c = (0+j5)\Omega$. Find the line currents and the current through the neutral. (9)

OR


18. a) Impedances Z_2 and Z_3 in parallel are connected in series with an impedance Z_1 across a 100V, 50Hz ac supply. $Z_1 = (6.25+j1.25)\Omega$, $Z_2 = 5\Omega$, $Z_3 = (5 - jX_c)\Omega$. Determine the value of capacitance of X_c such that the total current of the circuit will be in phase with the total voltage. (7)
- b) A three phase, 4-wire, 208V CBA system is connected to a star connected load with $Z_A = 5\angle 0^\circ \Omega$, $Z_B = 5\angle 30^\circ \Omega$, $Z_C = 10\angle -60^\circ \Omega$. Obtain the phase currents and the current through neutral wire. (7)

MODULE V

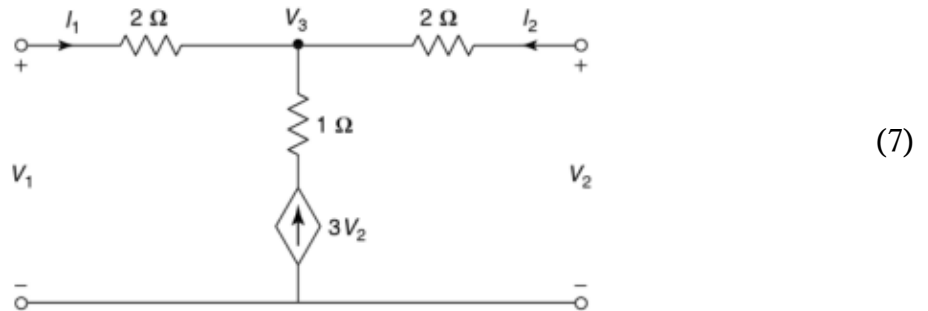19. a) Find the Y parameters of the network given below.




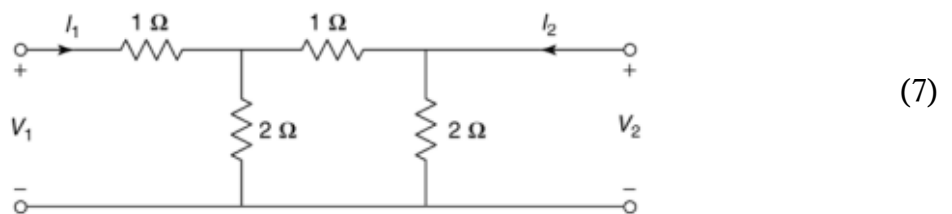- b) Obtain the ABCD parameters of the network given below.



OR

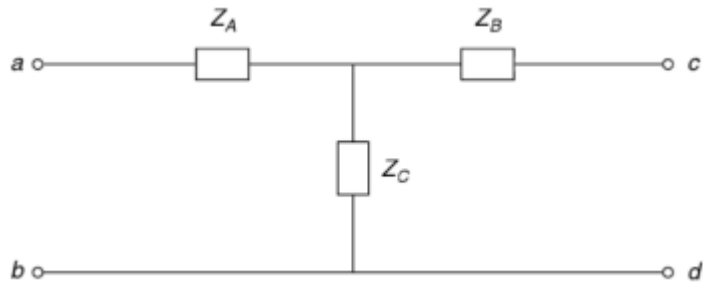20. a) A network has two input terminals (a, b) and two output terminals (c, d) as shown in the figure given below. The input impedance with c and d open circuited is $(250+j100)\Omega$ and with c and d short circuited is $(400+j300)\Omega$. The impedance across c and d with a and b open circuited is 200 Ω . Determine the equivalent T- network parameters. (9)



- b) Derive the conditions for symmetry and reciprocity in a two port network for a ABCD parameters. (5)
