

G 1551

(Pages : 2)

Reg. No.....

Name.....

B.TECH. DEGREE EXAMINATION, MAY 2016

Fourth Semester

Branch : Applied Electronics and Instrumentation / Electronics and Communication / Electronics and Instrumentation / Instrumentation and Control Engineering

AI 010 404 / EC 010 404 / EI 010 404 / IC 010 404 – DIGITAL ELECTRONICS [AI, EC, EI, IC]

(New Scheme – 2010 Admission onwards)

[Regular/Improvement/Supplementary]

Time : Three Hours


Maximum : 100 Marks

Part A

Answer all questions.

Each question carries 3 marks.

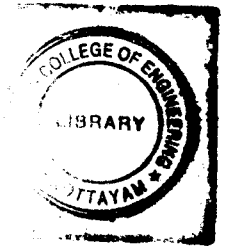1. Explain the Duality theorem.
2. Explain NMOS NOR gate.
3. Design a half adder circuit.
4. Mention some applications shift register.
5. Explain different types of ROM.



(5 × 3 = 15 marks)

Part B

Answer all questions.

Each question carries 5 marks.

6. What is meant by error code?
7. Explain the terms fan-in and fan-out.
8. Design a 1-bit comparator circuit.
9. What is a shift register?
10. Which are different types of PLDs?

(5 × 5 = 25 marks)

Turn over

Part C*Answer all questions.**Each full question carries 12 marks.*

11. Minimize the Boolean expression

$$f = \sum m (3, 4, 7, 9, 10, 11) + d (0, 1, 2, 13, 14, 15)$$

using SOP and POS.

Or

12. (a) Write notes on different number systems.
 (b) What is meant by parity?

(6 + 6 = 12 marks)

13. (a) Explain TTL logic circuit.
 (b) Draw and explain CMOS inverter circuit.

(6 + 6 = 12 marks)

Or

14. (a) What is meant by emitter coupled logic?
 (b) Explain the terms propagation delay, noise margin.

(6 + 6 = 12 marks)

15. Design a 8 : 1 multiplexer using 4 : 1 multiplexer.

Or

16. (a) What is a decoder circuit?
 (b) Draw and explain an asynchronous counter.

(6 + 6 = 12 marks)

17. (a) Design a mod-5 counter.
 (b) Explain different types of shift registers.

(6 + 6 = 12 marks)

Or

18. (a) What is meant by a universal register?
 (b) Explain some applications of flip-flop.

(6 + 6 = 12 marks)

19. Explain the architecture of FPGA.

Or

20. (a) Which are different types of hazards?
 (b) What is the difference between PAL and PLA?

(6 + 6 = 12 marks)

[5 × 12 = 60 marks]

