

Register No.: .....

Name : .....

**SAINTGITS COLLEGE OF ENGINEERING (AUTONOMOUS)**

(AFFILIATED TO APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY, THIRUVANANTHAPURAM)

**SIXTH SEMESTER B.TECH DEGREE EXAMINATION (R), MAY 2023****ELECTRONICS AND COMMUNICATION ENGINEERING****(2020 SCHEME)****Course Code : 20ECT308****Course Name : Comprehensive Course Work****Max. Marks :50****Duration : 75 Minutes****PART A****(Answer all questions. Each question carries 1 mark)**

- 1 For a full wave rectifier, with sinusoidal input and inductor as filter, ripple factor for maximum load current and minimum load current conditions are respectively  
**A.** 0.1 and 1 **B.** 0.1 and 0.47  
**C.** 0 and 0.47 **D.** 0 and 0.22
- 2 An amplifier has a power gain of 100. Its db gain is .....  
**A.** 10dB **B.** 20dB  
**C.** 40dB **D.** 0dB
- 3 The voltage gain of an amplifier is 100. A negative feedback is applied with  $\beta=0.03$ . The overall gain of the amplifier  
**A.** 70 **B.** 25  
**C.** 99.97 **D.** 3
- 4 The voltage gain of an amplifier without feedback and with negative feedback respectively is 100 and 20. The percentage of negative ( $\beta$ ) would be  
**A.** 4% **B.** 5%  
**C.** 20% **D.** 80%
- 5 If  $V_{cc} = 18V$ , voltage divider resistance  $R_1 = 4.7K\Omega$  and  $R_2 = 1500\Omega$ , what is the base bias voltage ?  
**A.** 8.70V **B.** 4.35V  
**C.** 2.9V **D.** 0.70V
- 6 An oscillator employs ..... feedback  
**A.** Positive **B.** Negative  
**C.** Neither positive nor negative **D.** Data insufficient
- 7 A full adder can be made out of .....  
**A.** two half adders **B.** two half adders and a OR gate  
**C.** two half adders and a NOT gate **D.** three half adders
- 8 For Emitter Coupled Logic (ECL), the switching speed is very high because  
**A.** Negative logic is used **B.** The transistors are not saturated when they are conducting  
**C.** Multi emitter transistors are used **D.** Low fan out
- 9 The product of which of the following gives the figure of merit of a logic family?  
**A.** Gain and bandwidth **B.** Propagation delay time and power dissipation  
**C.** Fan-out and propagation delay time **D.** Noise margin and power dissipation
- 10 The 2's complement representation of -17 is  
**A.** 100001 **B.** 101111  
**C.** 110011 **D.** 101110

- 11 A digital circuit that can store only one bit is a  
**A.** Register **B.** NOR gate  
**C.** Flip-flop **D.** XOR gate
- 12 Which logic family is the fastest?  
**A.** DTL **B.** CMOS  
**C.** TTL **D.** ECL
- 13 For a given op-amp, CMRR= $10^5$  and differential gain= $10^5$ . What is the common mode gain of the op-amp?  
**A.** infinity **B.**  $10^5$   
**C.**  $2 \times 10^5$  **D.** 1
- 14 In a circuit, if the open loop gain is  $10^6$  and output voltage is 10V, the differential voltage should be  
**A.**  $10 \mu\text{v}$  **B.** 0.1 v  
**C.**  $100 \mu\text{v}$  **D.**  $1 \mu\text{v}$
- 15 How many bits will a D/A converter use so that its full scale output voltage is 5V and its resolution is at the most 10mV  
**A.** 5 **B.** 7  
**C.** 9 **D.** 11
- 16 The large signal bandwidth of an op-amp is limited by its  
**A.** CMRR **B.** Slew rate  
**C.** Gain-bandwidth product **D.** Input impedance
- 17 A  $1 \mu\text{s}$  pulse can be stretched into a 1 ms pulse by using  
**A.** A mono stable multi vibrator **B.** An astable multi vibrator  
**C.** A bistable multi vibrator **D.** A JK flip flop
- 18 Which one of the following circuits is used for converting a sine wave into a square wave?  
**A.** Astable multi vibrators **B.** Mono stable multi vibrators  
**C.** Bistable multi vibrators **D.** Schmitt trigger
- 19 For an N point FFT algorithm with  $N=2^m$ , which one of the following statement is true?  
**A.** It is not possible to construct a signal flow graph with both input and output in normal order **B.** The number of butterflies in the  $m^{\text{th}}$  stage is  $N/m$   
**C.** In-place computation requires storage of only  $2N$  node data **D.** Computation of a butterfly requires only one complex multiplication
- 20 The transformation technique in which there is one to one mapping from s-domain to z-domain is  
**A.** Approximation of derivatives **B.** Impulse invariance method.  
**C.** Bilinear transformation method **D.** Backward difference for the derivative
- 21 Which of the following methods are used to convert analog filter into digital filter?  
**A.** Approximation of Derivatives **B.** Bilinear transformation  
**C.** Impulse invariance **D.** All of the mentioned
- 22 What is the process of increasing the sampling rate by a factor I?  
**A.** Sampling rate conversion **B.** Decimation  
**C.** Interpolation **D.** None of the mentioned


- 23 A digital filter is said to be an IIR if:
- A.** It oscillates **B.** All its poles lies outside unit circle  
**C.** Present output depends on previous output **D.** One or more denominator coefficient is zero
- 24 What is another term used for time scaling operation in digital signal processing?
- A.** Upsampling **B.** Downsampling  
**C.** Convolution **D.** Quantisation
- 25 A communication channel disturbed by Gaussian noise has a bandwidth of 6kHz and S/N ratio of 15. The maximum transmission rate that such a channel can support is
- A.** 2.4 kbits/sec **B.** 24 kbits/sec  
**C.** 32 kbits/sec **D.** 48 kbits/sec
- 26 If the modulating frequency of a carrier wave varies between 700Hz and 7KHz, find its bandwidth?
- A.** 10 KHz **B.** 23 KHz  
**C.** 17.3 KHz **D.** 12.6 KHz
- 27 The minimum bandwidth of the link needed for a guard band of 10kHz frequency to prevent interference between six channels, each with 100kHz frequency is
- A.** 425kHz **B.** 575kHz  
**C.** 650kHz **D.** 725kHz
- 28 If we correlate the received signal with any one of the two orthogonal function, the obtained inner product will be
- A.** In phase **B.** Quadrature  
**C.** Zero **D.** Cannot be determined
- 29 In delta modulation, the slope overload distortion can be reduced by
- A.** Decreasing the step size **B.** Decreasing the granular noise  
**C.** Decreasing the sampling rate **D.** Increasing the step size
- 30 The probability cumulative distribution function must be monotone and
- A.** increasing **B.** decreasing  
**C.** Non decreasing **D.** Non increasing

### **PART B**

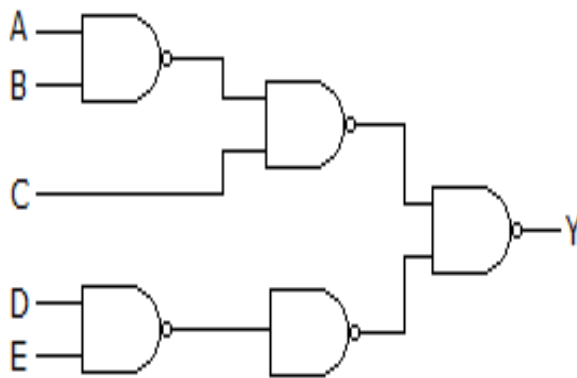**(Answer all questions. Each question carries 2 marks)**

- 31 The total gain of a multistage amplifier is less than the product of the gains of individual stages due to .....
- A.** Power loss in the coupling device **B.** Loading effect of the next stage  
**C.** The use of many transistors **D.** The use of many capacitors
- 32 The two stages of a cascade amplifier have individual upper cut-off frequencies  $f_1=5\text{MHz}$  and  $f_2=3.33\text{MHz}$ . What is the best approximation for the upper cut-off frequency in cascade combination?
- A.** 4.16MHz **B.** 3.33MHz  
**C.** 2.5MHz **D.** 5MHz
- 33 A 4 bit ripple counter and a 4 bit synchronous counter are made using flip flops having a propagation delay of 10ns each. If the worst-case delay in the ripple counter and the synchronous counter be R and S respectively, then
- A.**  $R=10\text{ns}$ ,  $S=40\text{ ns}$  **B.**  $R=40\text{ns}$ ,  $S=10\text{ ns}$   
**C.**  $R=10\text{ns}$ ,  $S=30\text{ ns}$  **D.**  $R=30\text{ns}$ ,  $S=10\text{ ns}$

34 The circuit of the given figure realizes the function .....



- A.**  $Y = (\bar{A} + \bar{B})C + \bar{D}\bar{E}$
- B.**  $Y = \bar{A} + \bar{B} + \bar{C} + \bar{D} + \bar{E}$
- C.**  $AB + C + DE$
- D.**  $AB + C(D+E)$

35 The frequency of oscillation of astable multivibrator with component values  $R_1 = 2K\Omega$   $R_2 = 20K\Omega$   $C_1 = 0.01\mu F$  ,  $C_2 = 0.05\mu F$  is

- A.** 1428.5 Hz
- B.** 142.85 Hz
- C.** 14.285 Hz
- D.** 1.4285 Hz

36 What is the maximum frequency for sine wave output voltage of 10v peak with an Op-amp whose slew rate is  $1V/\mu s$ ?

- A.** 15.92kHz
- B.** 19.73kHz
- C.** 23.54kHz
- D.** 27.336kHz

37 What is the folding frequency for the aliased version of  $x(n)$  with sampling rate  $F$ ?

- A.**  $F/D$
- B.**  $F/4D$
- C.**  $F/2$
- D.**  $F/2D$

38 The 4-point Discrete Fourier Transform (DFT) of a discrete time sequence  $\{1,0,2,3\}$  is

- A.**  $[0, -2+2j, 2, -2-2j]$
- B.**  $[2, 2+2j, 6, 2-2j]$
- C.**  $[6, 1-3j, 2, 1+3j]$
- D.**  $[6, -1+3j, 0, -1-3j]$

39 In Delta modulation \_\_\_\_\_

- A.** all the coded bits used for sampling are transmitted
- B.** one bit per sample is transmitted
- C.** the step size is fixed
- D.** Both A & B

40 A bandwidth of 10kHz is required for AM system. If the lowest frequency component in the modulated signal is 555kHz, carrier frequency in kHz is

- A.** 525
- B.** 550
- C.** 560
- D.** 565