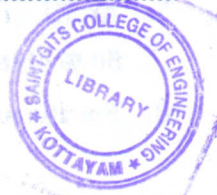


B.TECH. DEGREE EXAMINATION, NOVEMBER 2014**Third Semester**

Branch : Electrical and Electronics Engineering
 EE 010 303—ELECTRIC CIRCUIT THEORY (EE)
 (New Scheme—2010 Admission onwards)
 [Regular/Improvement/Supplementary]



Time : Three Hours

Maximum : 100 Marks

Part A

*Answer all question briefly.
 Each question carries 3 marks.*


1. Explain the differences between dependent and independent sources.
2. The natural frequencies of a linear time invariant network are given by $s_1 = -2 + j3$ and $s_2 = -2 - j3$. Give expressions for step response.
3. Define the following with reference to network topology :
 - (a) Tree.
 - (b) Branch.
 - (c) Oriented graph.
4. List the properties of Hurwitz polynomial.
5. A 3-wire, 3-phase supply feeds a load consisting of 3 equal resistors. By how much is the load reduced if one of the resistors is removed, if the load is star connected.

(5 × 3 = 15 marks)

Part B

*Answer all questions.
 Each question carries 5 marks.*

6. Calculate the open circuit voltage v_{oc} in the circuit shown in Fig. 1.

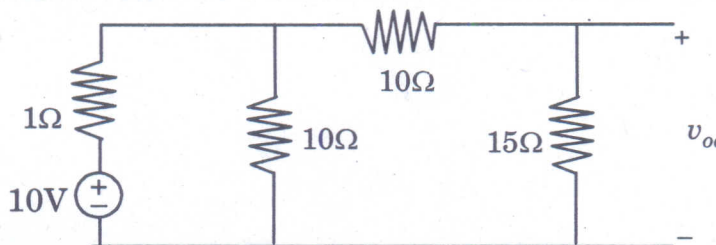**Fig. 1****Turn over**

7. An RL circuit has $R = 2\Omega$ and $L = 4H$. Find the time required for the inductor current to reach 50 % of its steady state value.
8. For the network graph shown in Fig. 2, select a tree T (1, 2, 3, 4) and write the basic cut-set matrix.

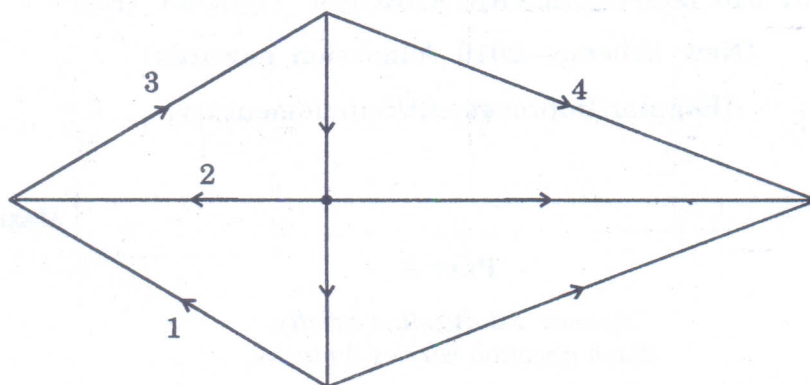


Fig. 2

9. Find V_o in the circuit in Fig.3

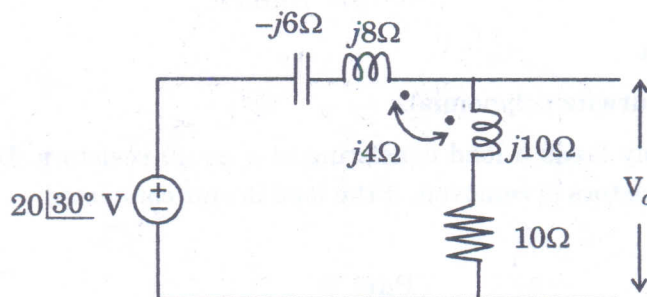


Fig. 3

10. Three equal star-connected inductors take 8 kW at power factor 0.8 when connected to a 415 V, 3-phase, 3 wire supply. Calculate the line currents when one inductor is short circuited.

(5 × 5 = 25 marks)

Part C

Answer all questions.
Each full question carries 12 marks.

11. (a) Find the current through the $1\ \Omega$ resistor in Fig. 4 using Millman's theorem.

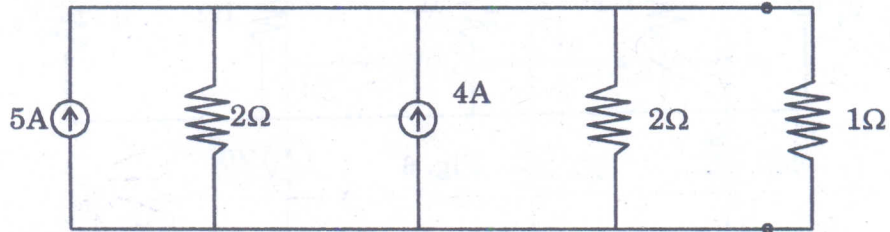


Fig. 4

(6 marks)

- (b) Check the validity of Tellegen's theorem provided

$$V_1 = 8V, V_2 = 4V, V_4 = 2V, I_1 = 4A, I_2 = 2A \text{ and } I_3 = 1A \text{ in Fig. 5}$$

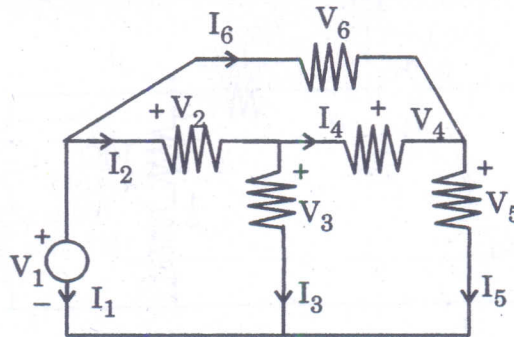


Fig. 5

Or

(6 marks)

Turn over

12. For the network shown in Fig. 6 determine the numerical values of (a) voltage transfer function
(ii) driving point impedance.

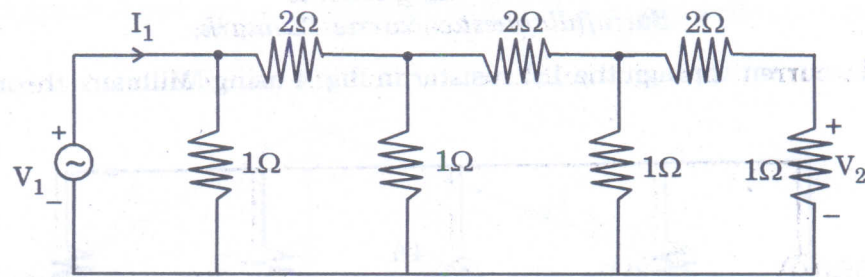


Fig. 6

13. With $V_s = 10$ volt, $R = 10 \Omega$, $L = 1$ H and $C = 1 \mu\text{F}$, $V_c(0^-) = 0$, find $i(0^+)$, $\frac{di}{dt}(0^+)$ and $\frac{d^2i}{dt^2}(0^+)$ for the series RLC circuit connected to the d.c. voltage at $t = 0$, where $i(t)$ is the current in the circuit.

Or

14. In the circuit shown in Fig 7, the switch K is closed at $t = 0$ with network previously unenergized. For the network element values shown in Fig. 7, find $i_1(t)$ and $i_2(t)$. Use Laplace Transform method.

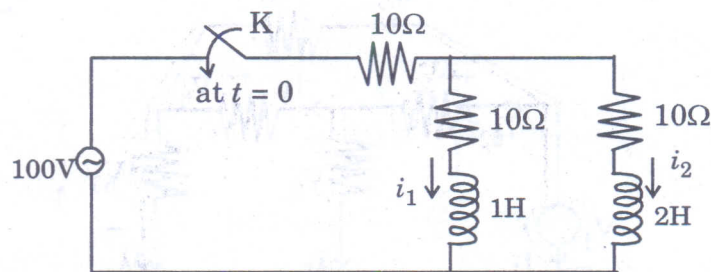


Fig. 7

15. For the network graph shown in Fig. 8, select a suitable tree and obtain the tie-set matrix. Hence write the Kirchoff's voltage law equations

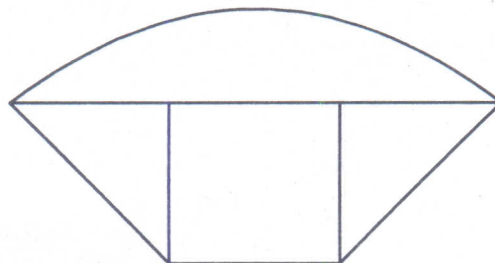


Fig. 8

Or

16. Find v_1 , v_2 and v_3 by node analysis, using MATAB program, for the network shown in Fig. 9.

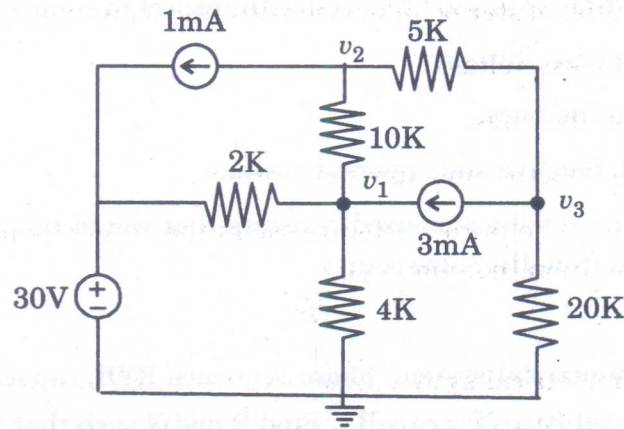


Fig. 9

17. Find $I_1(s)$ and $I_2(s)$ in the following circuit (Fig. 10)

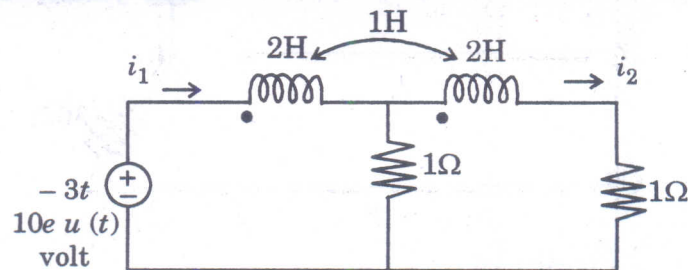


Fig. 10

Or

18. (a) Test whether $s^5 + 3s^4 + 3s^3 + 4s^2 + s + 1$ is Hurwitz or not. (6 marks)
- (b) Synthesise the admittance function $Y(s) = \frac{4s^2 + 6s}{s + 1}$. (6 marks)

Turn over

19. Three impedances $Z_A = 20 \angle 30^\circ \Omega$, $Z_B = 20 \angle -30^\circ \Omega$ and $Z_C = 20 \angle 60^\circ \Omega$ are connected in Y across a 400 V, 3 phase, 3 wire, ACB sequence symmetrical sources. Find :

- (i) The potential of star point of load with respect to supply neutral.
- (ii) The load phase voltage.
- (iii) Current in the lines.
- (iv) Total real, reactive and apparent powers.
- (v) The balanced delta connected resistors that would take the same real power as the above load from the same source.

Or

20. (a) In a 3-phase symmetrical system, phase sequence RYB, capacitive reactance $X_C = 10\Omega$ is across YB and a coil $R + jX$ across RY. Find R and X such that $I_Y = 0$.
- (b) The circuit in Fig. 11 shows an infinite impedance (open circuit) in phase B of the star-connected load. Find the phasor voltage V_{OB} if the system is 208 volt, sequence ABC.

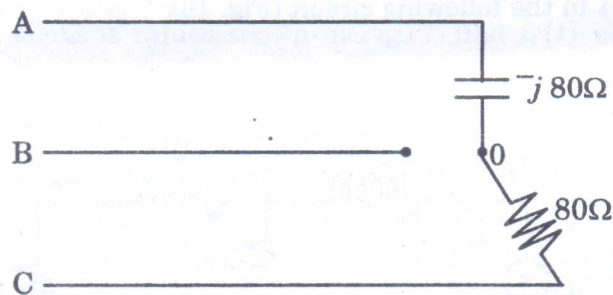


Fig. 11

(5 × 12 = 60 marks)

