

B.TECH. DEGREE EXAMINATION, MAY 2016**Fourth Semester**

Branch : Electrical and Electronics Engineering

NETWORK ANALYSIS AND SYNTHESIS (E)

(Old Scheme—Prior to 2010 Admissions)



[Supplementary/Mercy Chance]

Time : Three Hours

Maximum : 100 Marks

Part A*Answer all questions.**Each question carries 4 marks.*

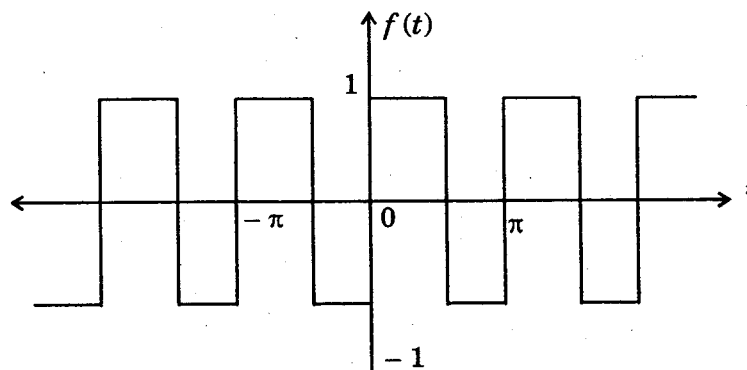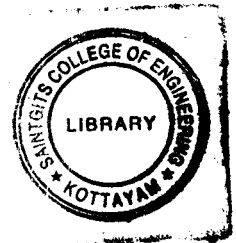1. State and explain initial value theorem.
2. Using definite integrals, find $L\{t^2\}$.
3. Illustrate the time shifting property of Fourier transform.
4. Find the complex Fourier coefficient of the following waveform :



5. Explain the procedure to obtain the admittance parameters of a 2-port network.
6. Obtain the relationship between Z and Y parameters.
7. The impedance parameters of a T-network are :
 $Z_{11} = 5\Omega, Z_{12} = Z_{21} = 2.5\Omega, Z_{22} = 10\Omega$. Find the parameters of the network.
8. What are the drawbacks of constant K filters ? How they are overcome ?

Turn over

9. What is meant by positive real functions? What are their properties?
10. What are the necessary and sufficient conditions for a real rational function $F(s)$ to be the driving point immittance of LC network?


(10 × 4 = 40 marks)

Part B

Answer all questions.


Each full question carries 12 marks.

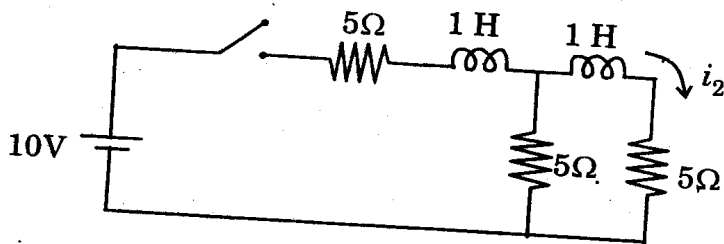11. Using Laplace transformation technique, find $i_2(t)$, following the switching at $t = 0$ in the circuit shown below. Assume zero initial conditions:



Or

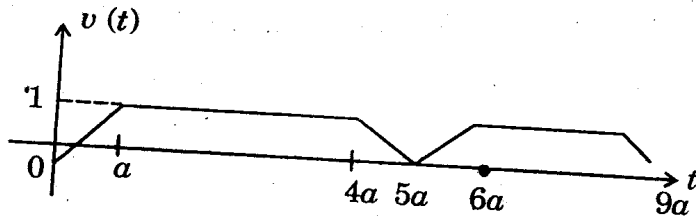
12. (i) Obtain the Laplace transform of the periodic waveform shown below:



(6 marks)


- (ii) Find the inverse Laplace transform of $\frac{48}{s^2(s+2)(s+4)}$.

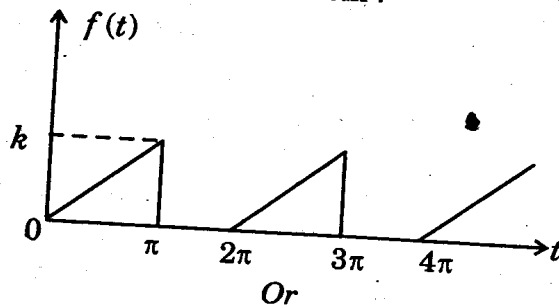13. Find the Fourier series of the following waveform:




Or

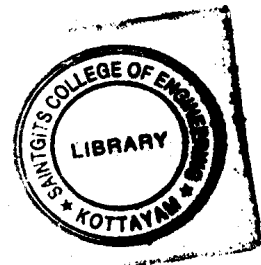14. Determine the Fourier transform of the exciting voltage $v(t) = \begin{cases} Ae^{-t}, & t \geq 0 \\ 0, & t < 0. \end{cases}$





(6 marks)

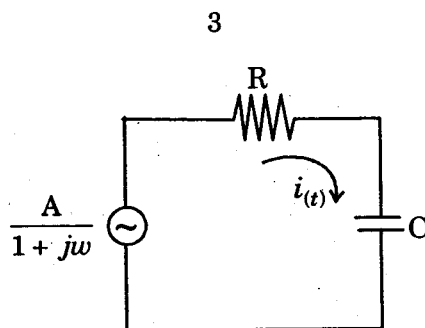

Also sketch the amplitude and phase spectrum. If the above voltage is applied across a series RC circuit, find $i(t)$.

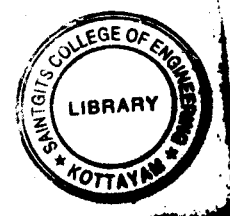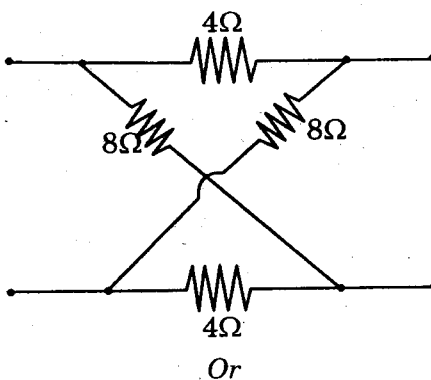15. Determine the z , h and ABCD parameters of the following lattice network :



16. A symmetrical π network has a series impedance of $10\ \Omega$ and shunt arm impedances of $5\ \Omega$. Determine :

- (i) The transmission parameters.
- (ii) The equivalent symmetrical T-network.

17. Design an image parameter based high-pass filter for a $1000\ \Omega$ load impedance to cut-off at $10,000\ \text{Hz}$ with infinite attenuation at $9000\ \text{Hz}$. Terminate with appropriate end sections.

Or

18. Derive the basic circuit of a constant-K band-pass filter. In terms of the parameters of this circuit, show an m -derived section. Explain the operation of this circuit.
19. Find the Foster network which will respond as follows : Poles at $\omega_2 = 6000$, $\omega_4 = 8000$ and infinity zeroes at $\omega_1 = 5000$, $\omega_3 = 7000$ and $\omega_5 = 9000$. Also the input impedance is $-j 1000$ at $\omega = 1000$.

Or

20. Realise using Cauer I and Cauer II forms, the driving point impedance $\frac{s^2 + 9s + 18}{s(s^2 + 5s + 4)}$. Draw the networks.

(6 + 6 = 12 marks)

[5 × 12 = 60 marks]