

F 3636

(Pages : 2)

Reg. No.....

Name.....



B.TECH. DEGREE EXAMINATION, NOVEMBER 2014

Fifth Semester

Branch : Electronics and Communication Engineering

EC 010 503—DIGITAL SYSTEM DESIGN (EC)

(New Scheme—2010 Admission onwards)

[Regular/Improvement/Supplementary]

Time : Three Hours

Maximum : 100 Marks

Part A

Answer all questions.

Each question carries 3 marks.

1. Define operators. List out the different types of operators.
2. Differentiate ROM and PLA ?
3. Define FSM ? Draw the block diagram of FSM.
4. List out the ASM chart components.
5. Define linear feedback shift register.

(5 × 3 = 15 marks)

Part B

Answer all questions.

Each question carries 5 marks.

6. Implement de-multiplexer using verilog.
7. Describe the typical ROM internal origination with neat diagram.
8. Explain Meta stability.
9. Write a short note on algorithmic state machine.
10. Write a Verilog code for up/down counter.

(5 × 5 = 25 marks)

Part C

Answer all questions.

Each full question carries 12 marks.

11. Write a short note on :
 - (i) Signal drivers.
 - (ii) Data types.
 - (iii) Language elements.

Or

Turn over

12. Design an encoder using two half adders by writing Verilog program.
13. Design using PLA the following Boolean functions.

(i) $X(A, B, C) = \sum(0, 1, 2, 4)$

(ii) $Y(A, B, C) = \sum(0, 5, 6, 7)$.

Or

14. Explain Quine–McCluskey algorithm in detail.
15. Design a sequence detector which detects the sequence “01110” using D flip–flops.

Or

16. Design a serial binary adder using delay flip–flops.
17. Design a sequence detector that produces an output 1 whenever the sequence 101101 is detected using ASM chart.

Or

18. Explain state assignments in detail.
19. What is barrel shifter ? Explain its principle. Using Verilog HDL, Model a 4–bit parallel shifter.

Or

20. Write a note on :

(i) FSM.

(ii) Linear feedback shift register.

(5 × 12 = 60 marks)

