

G 1105

(Pages : 2)

Reg. No.....

Name.....

B.TECH. DEGREE EXAMINATION, MAY 2016

Seventh Semester

Branch : Electrical and Electronics Engineering

ELECTRICAL DRIVES AND CONTROL (E)

(Old Scheme—Prior to 2010 Admissions)

[Supplementary/Mercy Chance]

Time : Three Hours

Maximum : 100 Marks

Part A

Answer all questions.

Each question carries 4 marks.

1. Explain the re-generative braking operation of a d.c. series motor.
2. Indicate how the load and motor characteristics determine the selection of appropriate drive.
3. What are the advantages and disadvantages of three-phase dual converter fed d.c. motor drives ?
4. What are the advantages of chopper fed d.c. drives ?
5. List the disadvantages of speed control of three-phase induction motors by stator voltage control.
6. What is meant by slip power recovery ?
7. Explain sinusoidal PWM.
8. What is freewheeling diode ?
9. Give different speed control schemes of synchronous motor.
10. What are the features of self-control of synchronous motors ?

(10 × 4 = 40 marks)

Part B

Answer all questions.

Each question carries 12 marks.

11. With the help of neat waveforms and diagrams explain the operation of fully controlled bridge rectifier drives.

Or

12. Describe the operation of a single-phase half wave controlled d.c. drive with necessary waveforms and diagrams.

Turn over

13. Describe the operation of a three-phase converter based d.c. drive which is suitable for four quadrant operation.

Or

14. Explain the armature voltage control of a d.c. motor using chopper drive.
15. Describe the slip power recovery with static Scherbius drive.

Or

16. Explain the V/F method for speed control of three-phase induction motor. What are its salient features?
17. Explain the operation of Voltage Source Inverter with neat diagram.

Or

18. Explain the operation of Current Source Inverter with neat circuit diagram.
19. Explain the operation of a self-controlled synchronous motor drive using load commutated thyristor inverter.

Or

20. Explain the open loop speed control of synchronous motor fed from voltage source inverters with neat diagram.

(5 × 12 = 60 marks)